

# Design Review

*PSEC3* 8-2-2010


## ADC

- digital structure
- specifications
- test points


Eric Oberla
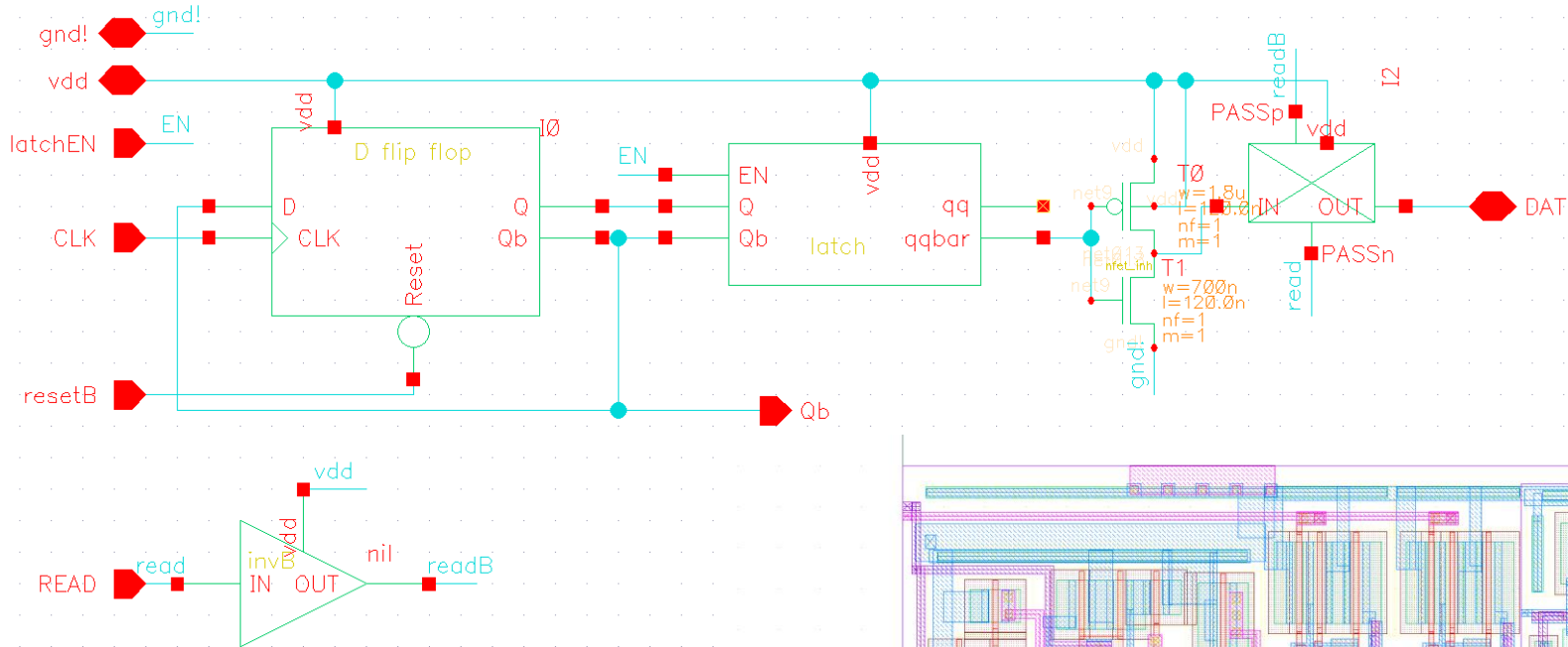
# ADC


Up to 12 bit Wilkinson ADC with 2 stage structure of counter+storage (fast dff+latch)



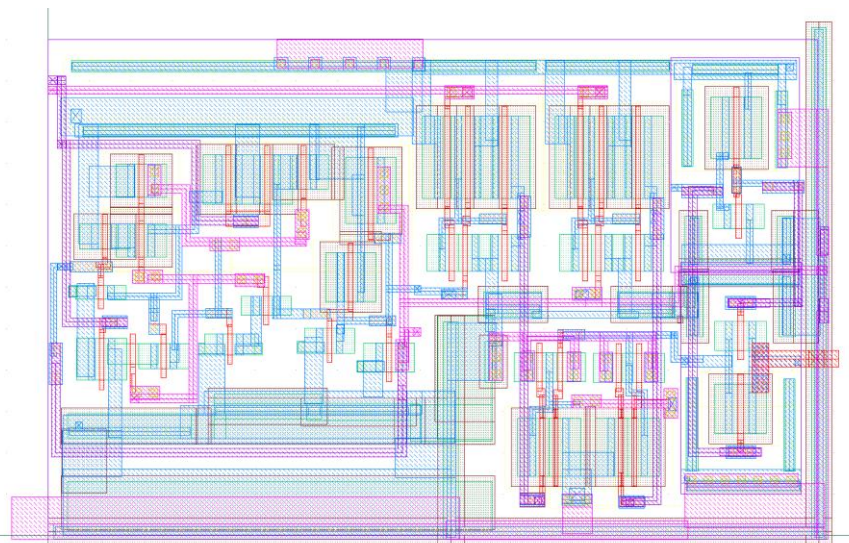In the future, this 2-stage structure could be tweaked to allow concurrent readout and digitization (would drastically reduce dead-time).



# ADC - latch

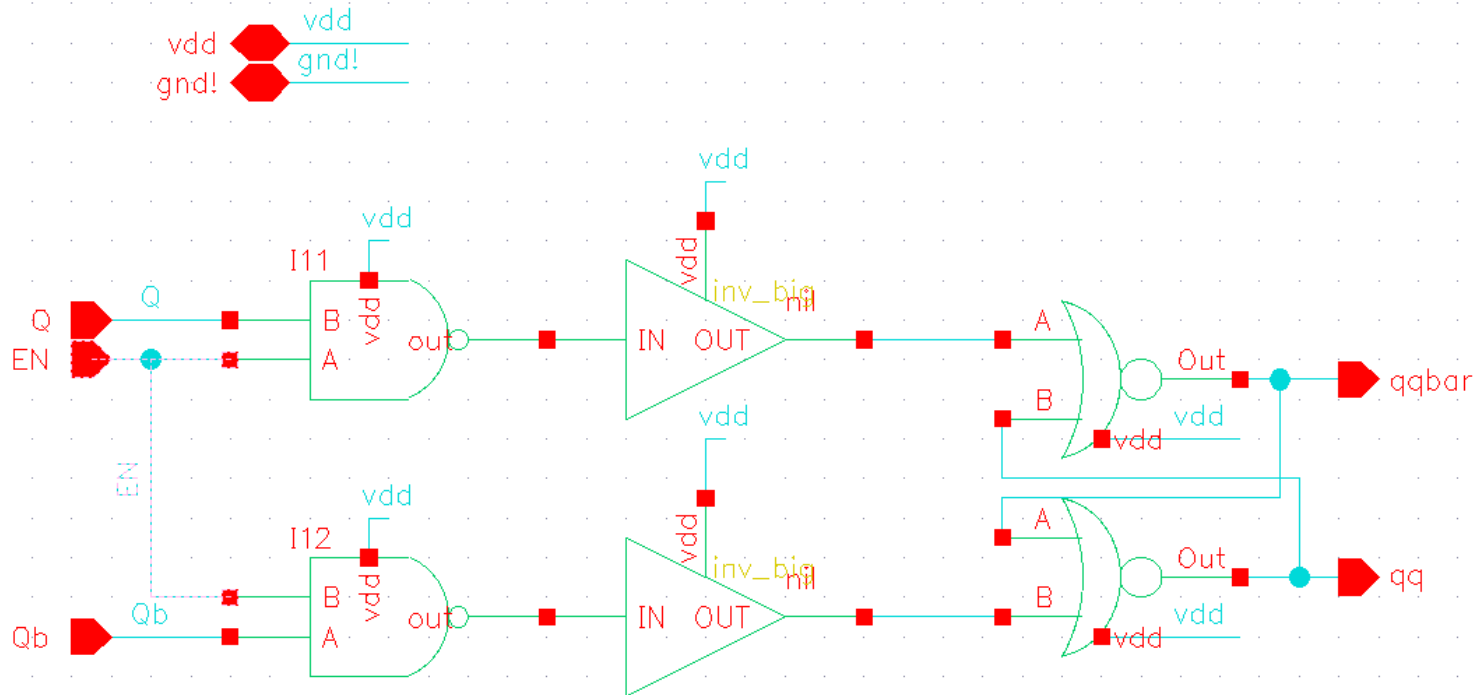


□ Standard NOR latch with Enable input follows fast d flip flop.

EN = 1 : latch is transparent


EN = 0 : latch stores last value

# ADC

One cell:

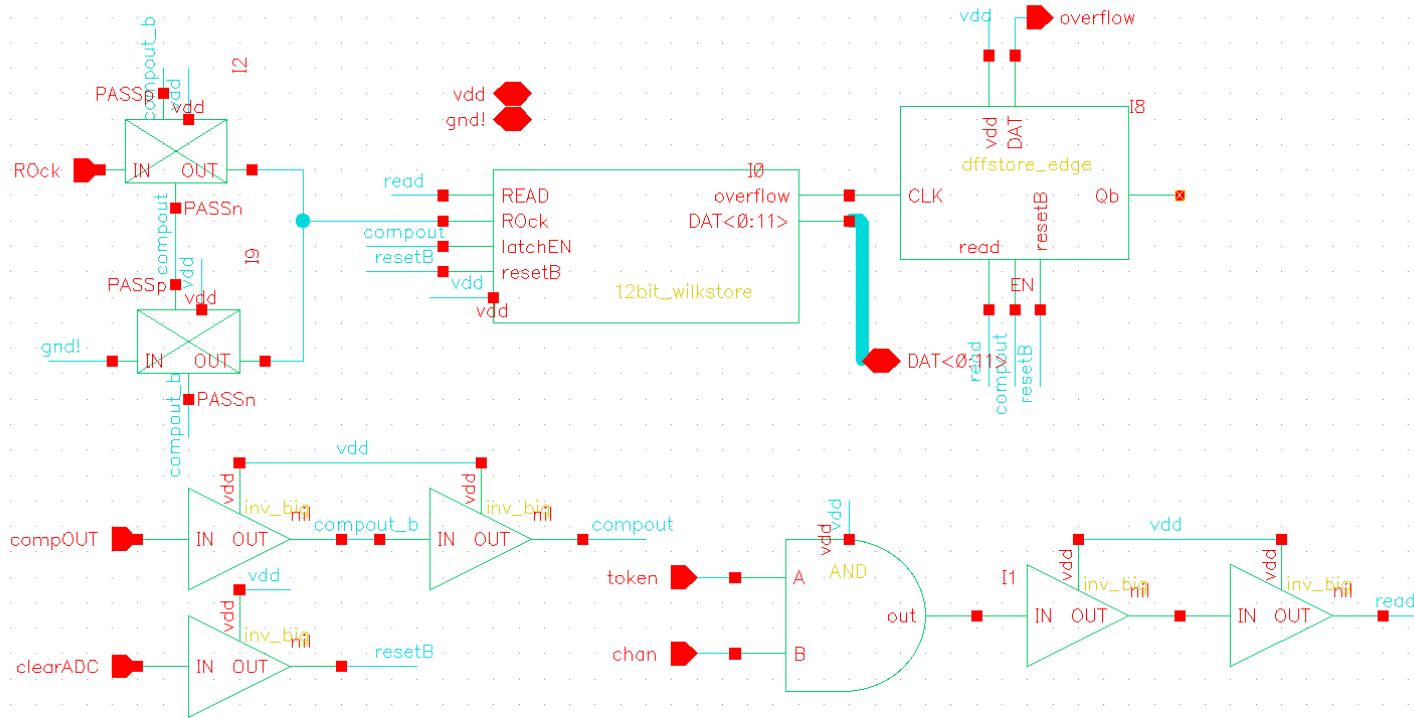


4-cell layout:

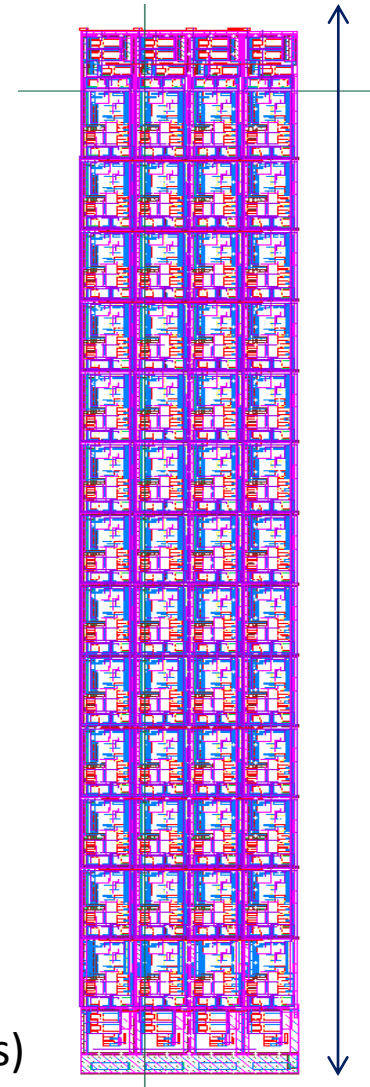

288 microns

- When running in 12 bit mode, notice of over-count given by overflow bit
- Cell's data addressed by Channel\_sel & Token\_sel. (more in readout slides)
- Counting and latch transparency controlled by comparator output

# simulation

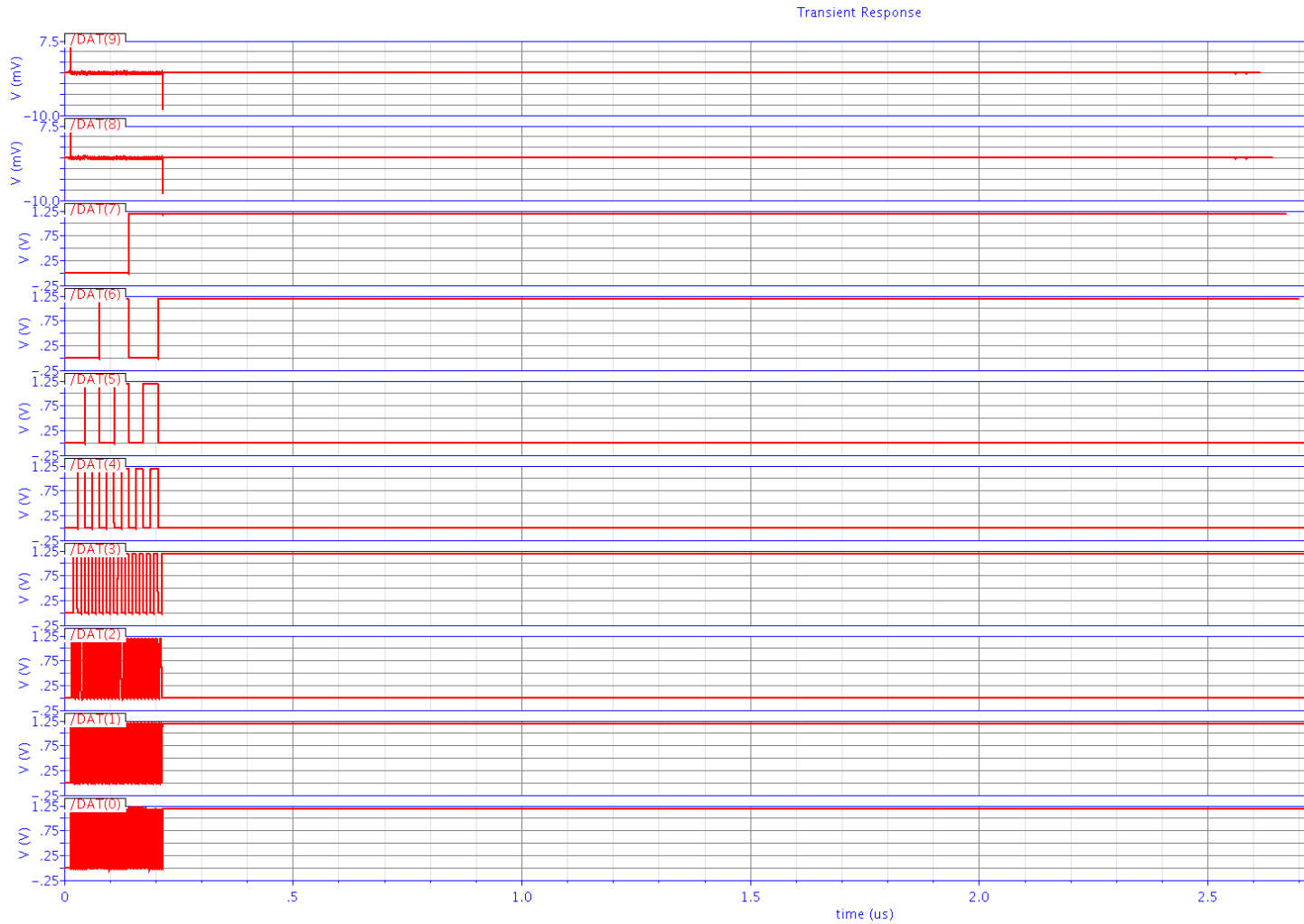


1GHz with comparator output = 200ns

DAT = 0b000011001011 == 203 counts (comparator rise+fall time)


# ring oscillator

- ~200MHz-2GHz clock generated on chip with ring oscillator
- 1 per channel + fan-out
- keep same structure as on PSEC2 - five stage inverter chain w/ positive feedback (analog controls on 2 stages)

Experimental results from PSEC2

 

# ring oscillator

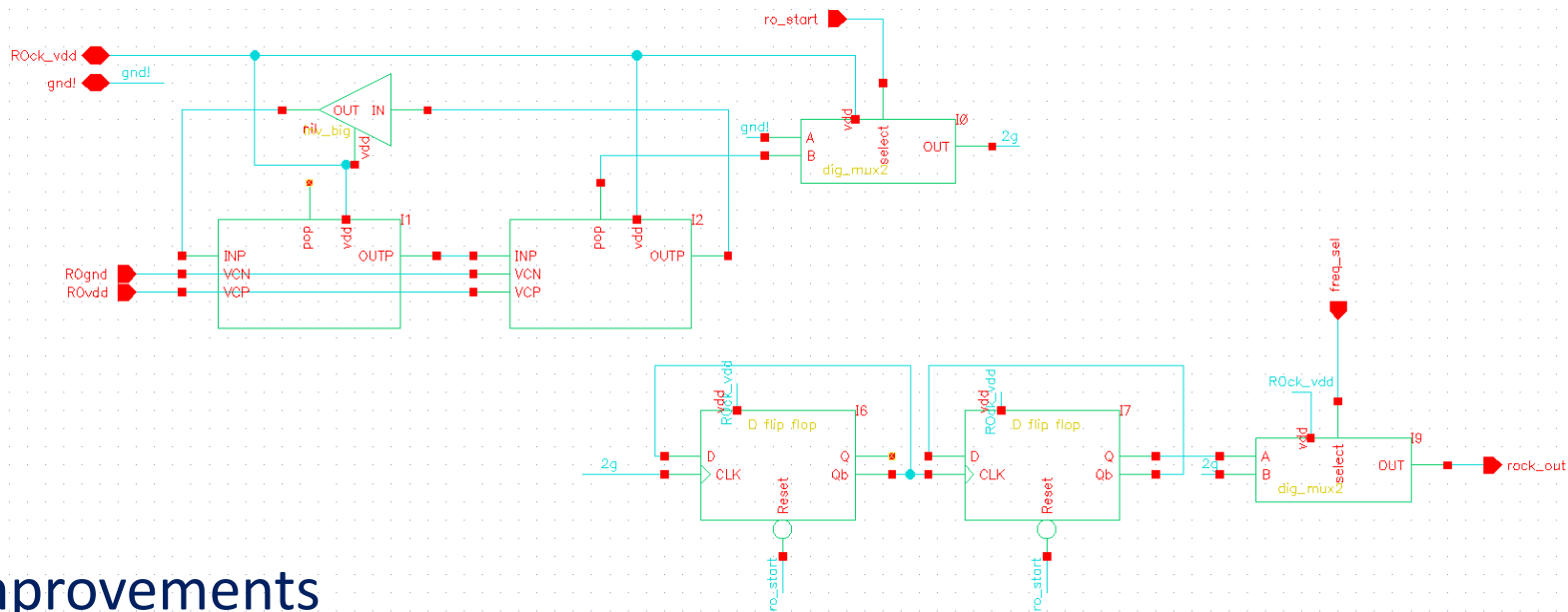


## improvements

- 'frequency select' option: duty cycle of RO departs from 50% @  $f < 1\text{GHz}$ , so to run slower, send 2GHz through divide-by-4 stage. Gives clean clock up to 500 MHz.
- 'RO\_enable' option: RO is free-running, but `RO_en` allows the fan-out drivers to be turned on/off (reducing noise).
 
# Clock fan-out

- fully simulated post-layout. Successfully distributes RO clock to 256 cells up to about 1.8 GHz.
- drivers can be turned off during sampling to reduce digital noise




Post-layout sim @ 800MHz



# noise considerations

- ADC can be completely turned off during sampling (except for ring oscillator)
- Complete structure surrounded by a 50 micron width of BFMOAT that gives ~130 Ohms of substrate resistance between other parts of chip.
- 'Large' decoupling cap (3.5 pF) near ring oscillator
- Upon extraction, 75 pF of parasitic capacitance between vdd and gnd
- Separate power rails for ADC and analog structures


# layout

 

# layout

Fan-out drivers

Ring oscillator

 

Data bus tri-state drivers  
(enabled by channel\_select)

