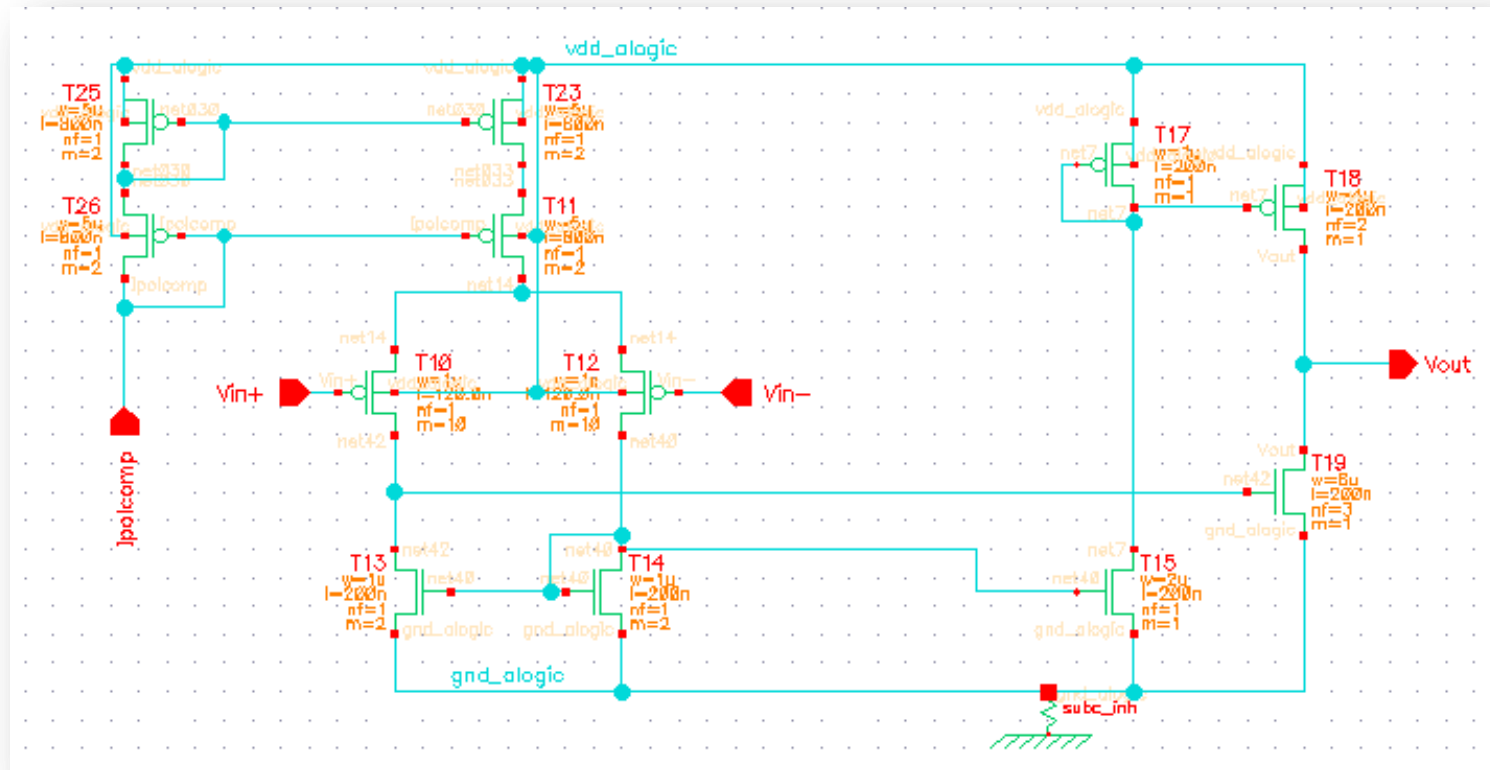


Comparator 1&2 and Ramp Buffer

Hervé Grabas




Comparator 1 – Schematic






Comparator gain

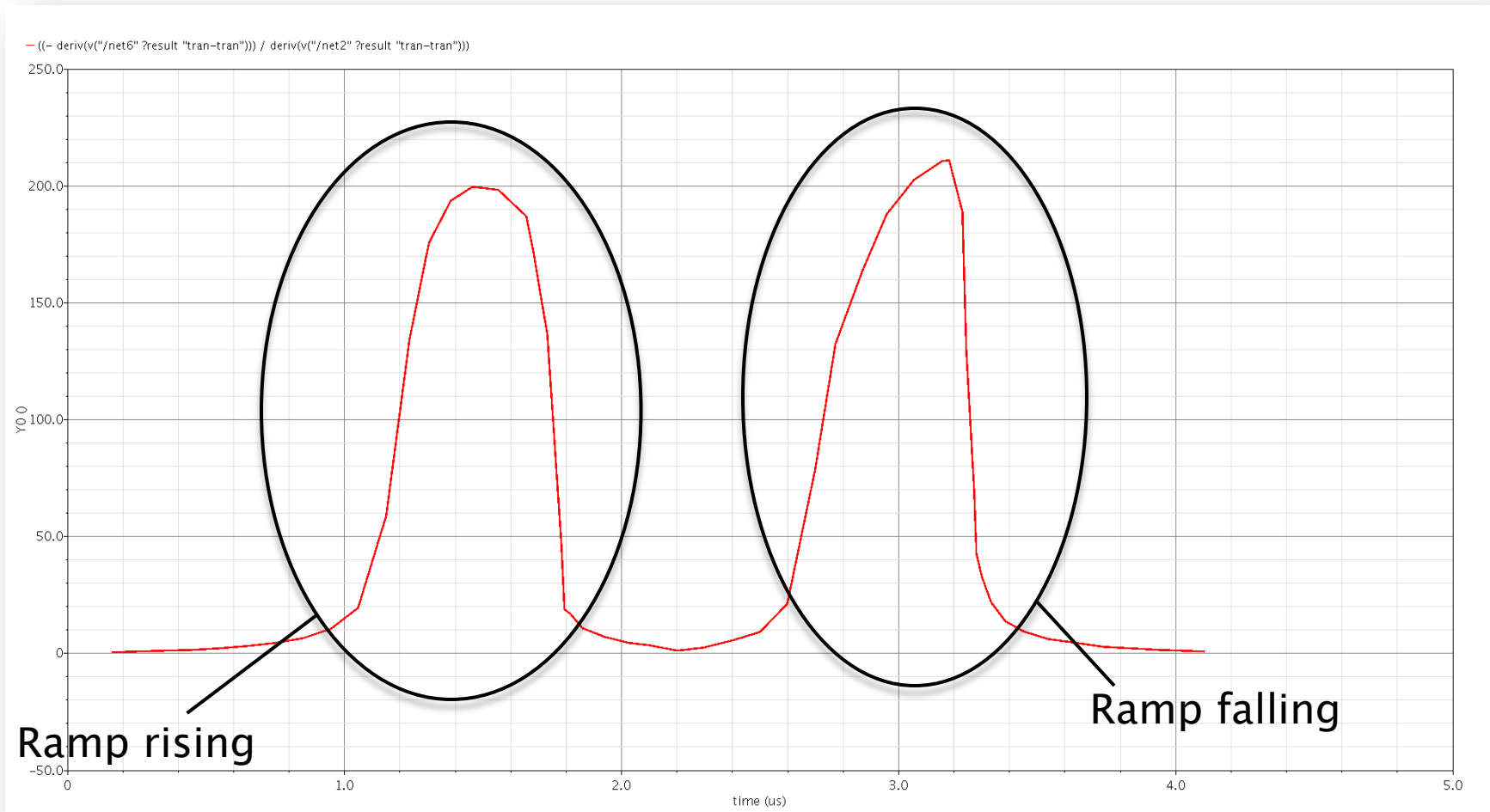



Comparator 1 – Layout

- ▶ Comparator size:
 $12\mu\text{m} \times 22\mu\text{m}$.
- ▶ Internal current source:
 $1\mu\text{A}$.
- ▶ 6.5fF output cap.
- ▶ 1 per cell: very
important offset.

 


Comparator 2 – Design

- ▶ The schematic of this comparator was very kindly given to us by Gerard and Jacque from LPC Clermont.
- ▶ It was modified to use less power and be smaller.



Comparator 2 – Schematic

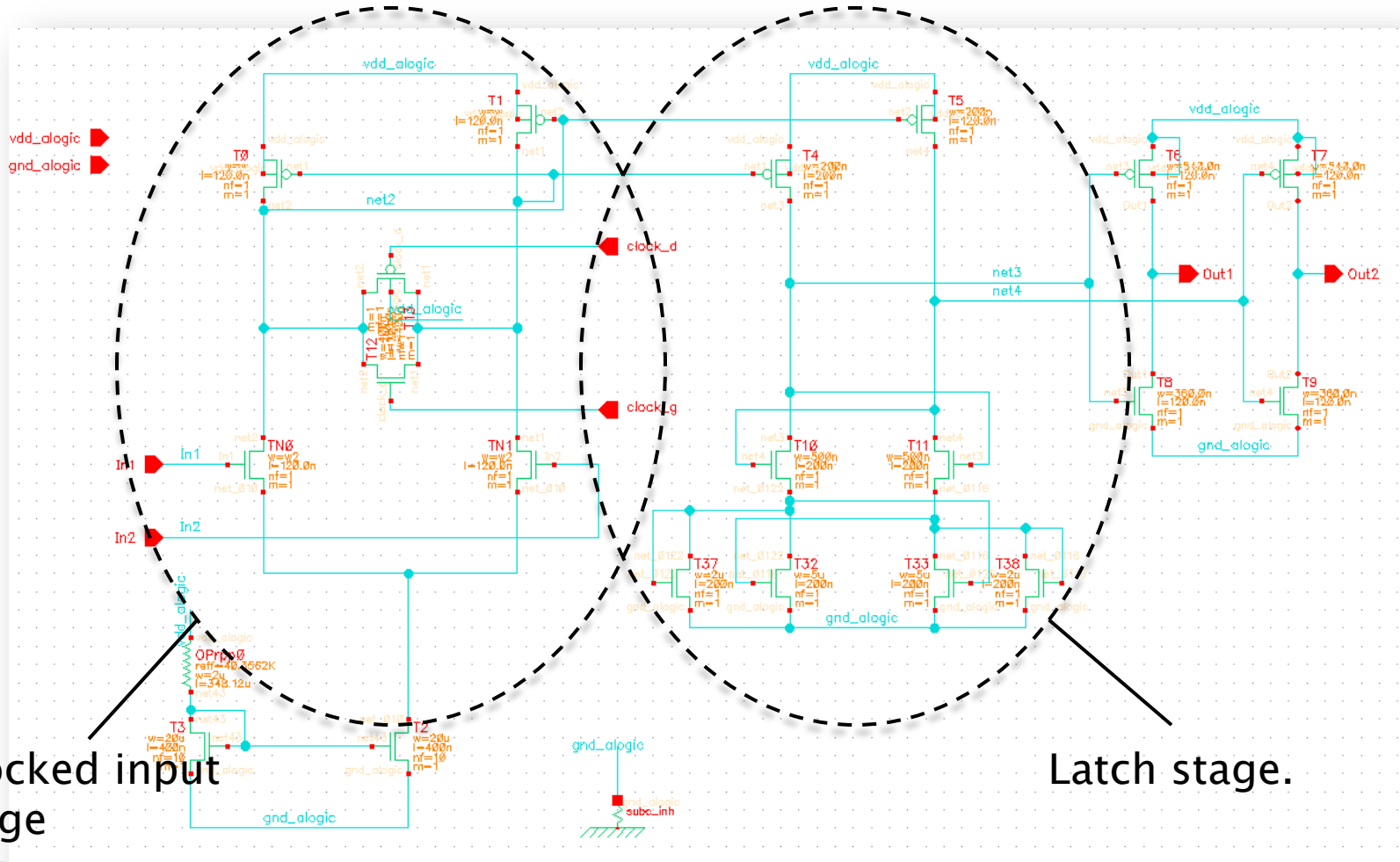

Clocked input stage

Latch stage.


Comparator 2 – Specification

- ▶ Will be tested on 5 & 6 channels.
- ▶ Clocked comparator. The clocked used is the clock of the ADC (Ring osc – see Eric's talk).
- ▶ Power consumption: 20uA.
- ▶ Layour not done so far.



Comparator 2 – Simulation

Transient Response

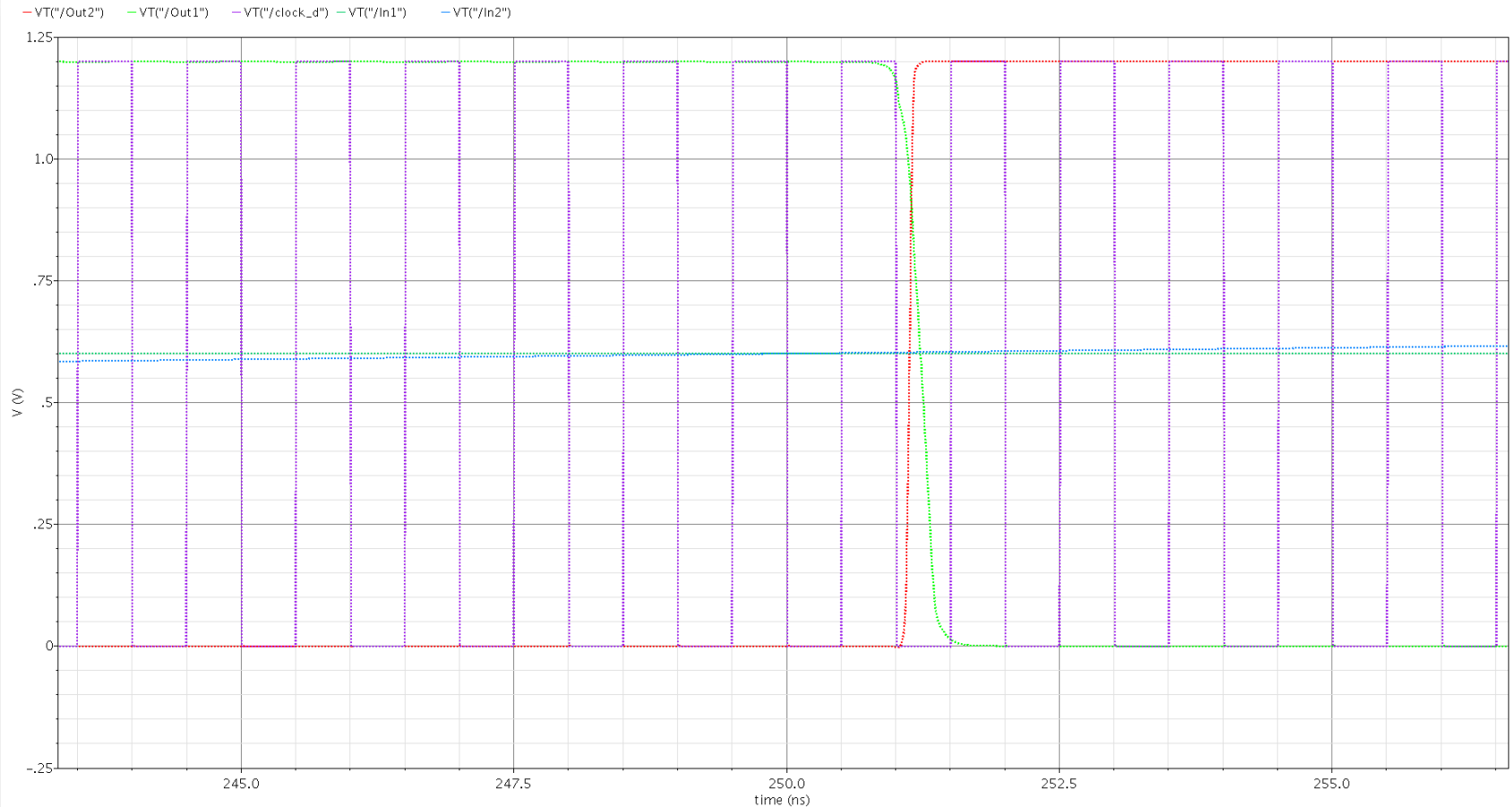


Working at 1GHz.



Comparator 2 gain

Transient Response


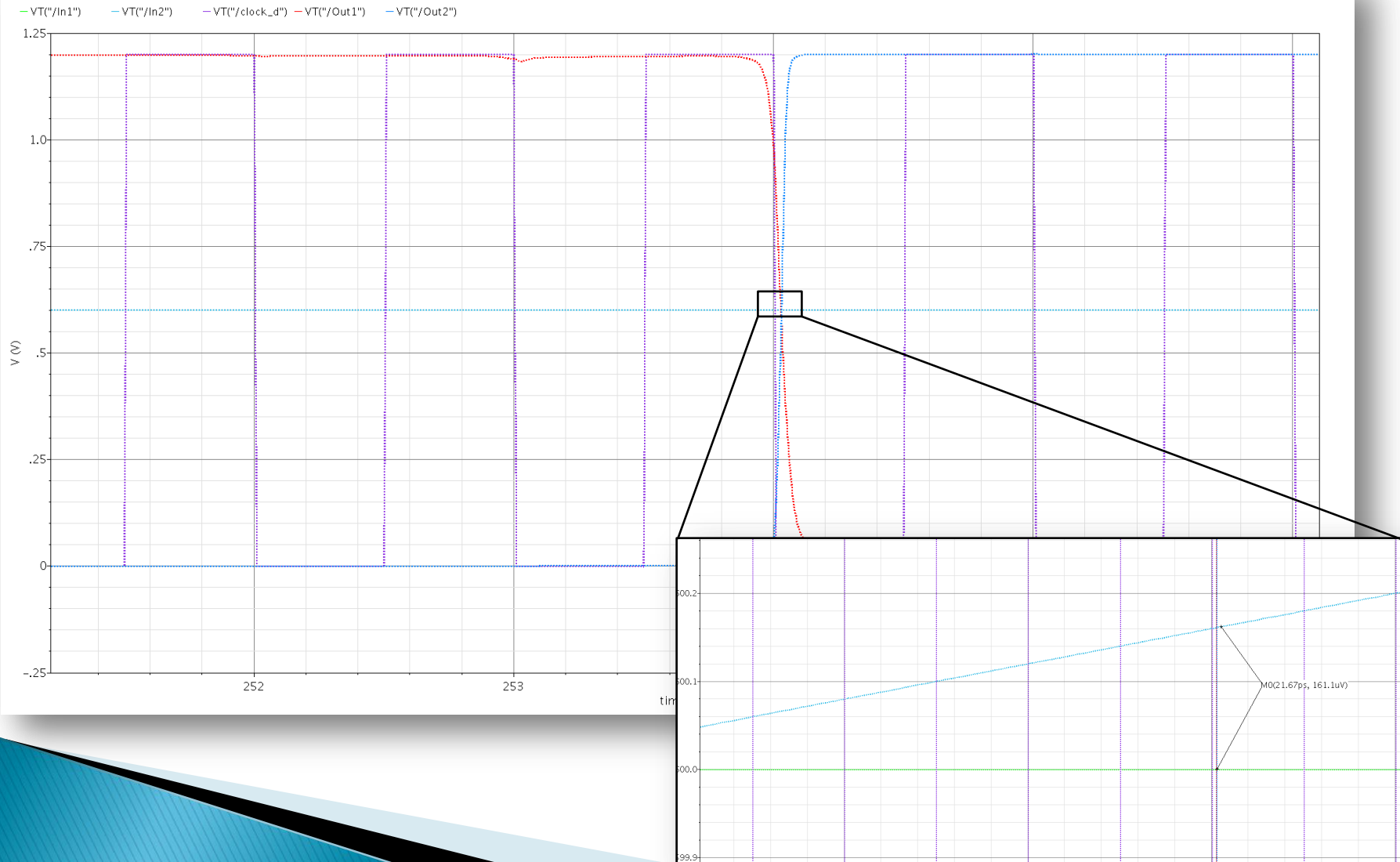


Ramp Buffer

- ▶ There is one ramp buffer per channel.
- ▶ Same design as the buffer for the sampling cell.
- ▶ Bigger output transistor.
- ▶ LvtPfets at the input to increase the linear range.




Ramp Buffer Schematic and Layout

 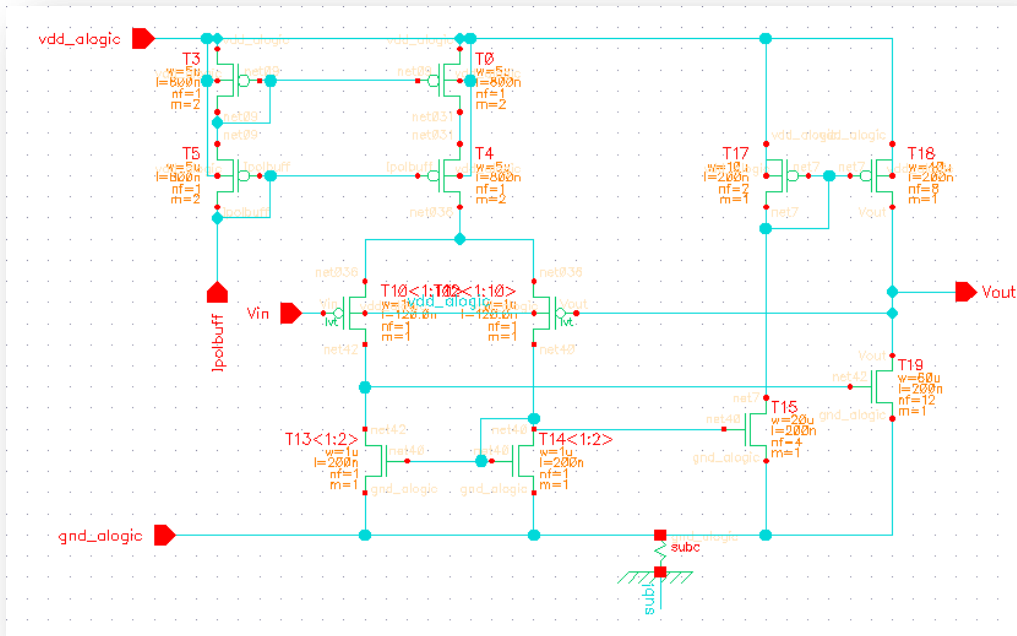

Layout size: $12\mu\text{m} \times 30\mu\text{m}$.
Internal current source: $1\mu\text{A}$

Driving capability

 

Simulation with a 10pF load.



Output integrated noise

