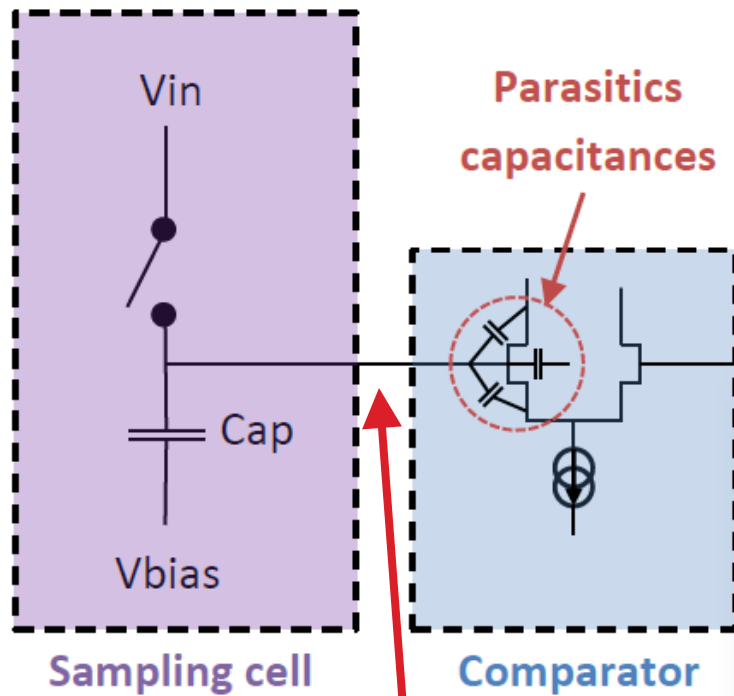


Fast Buffer Design

Hervé Grabas


The buffering question.



Buffer?

- Comparator parasitics capacitance value: 3.5fF

Capacitance

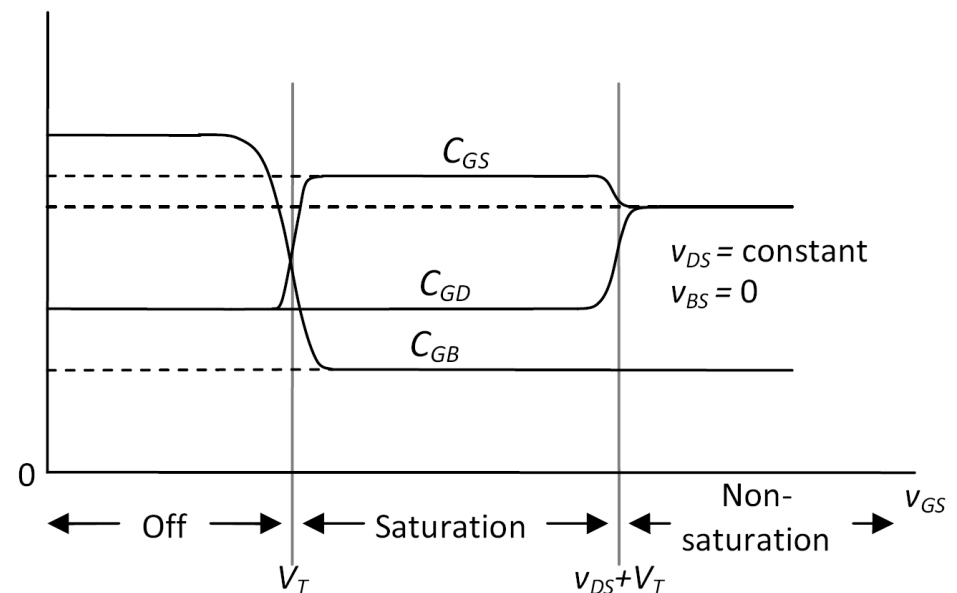


With and without buffer

	Without Buffer	With Buffer
Offset	Offset of the comparators	Offset of the comparators + buffers
Noise	Thermic noise of the 50 Ω	Noise of the buffer added
Readout delay	None	Buffering delay
Input dynamic	Maximum	Buffer dynamic
Linearity	Degraded by the parasitic capacitance of the comparator	Linearity of the buffer.

To answer the question : buffer in 4 channels. No buffers in 2 test channels.



Buffer schematic

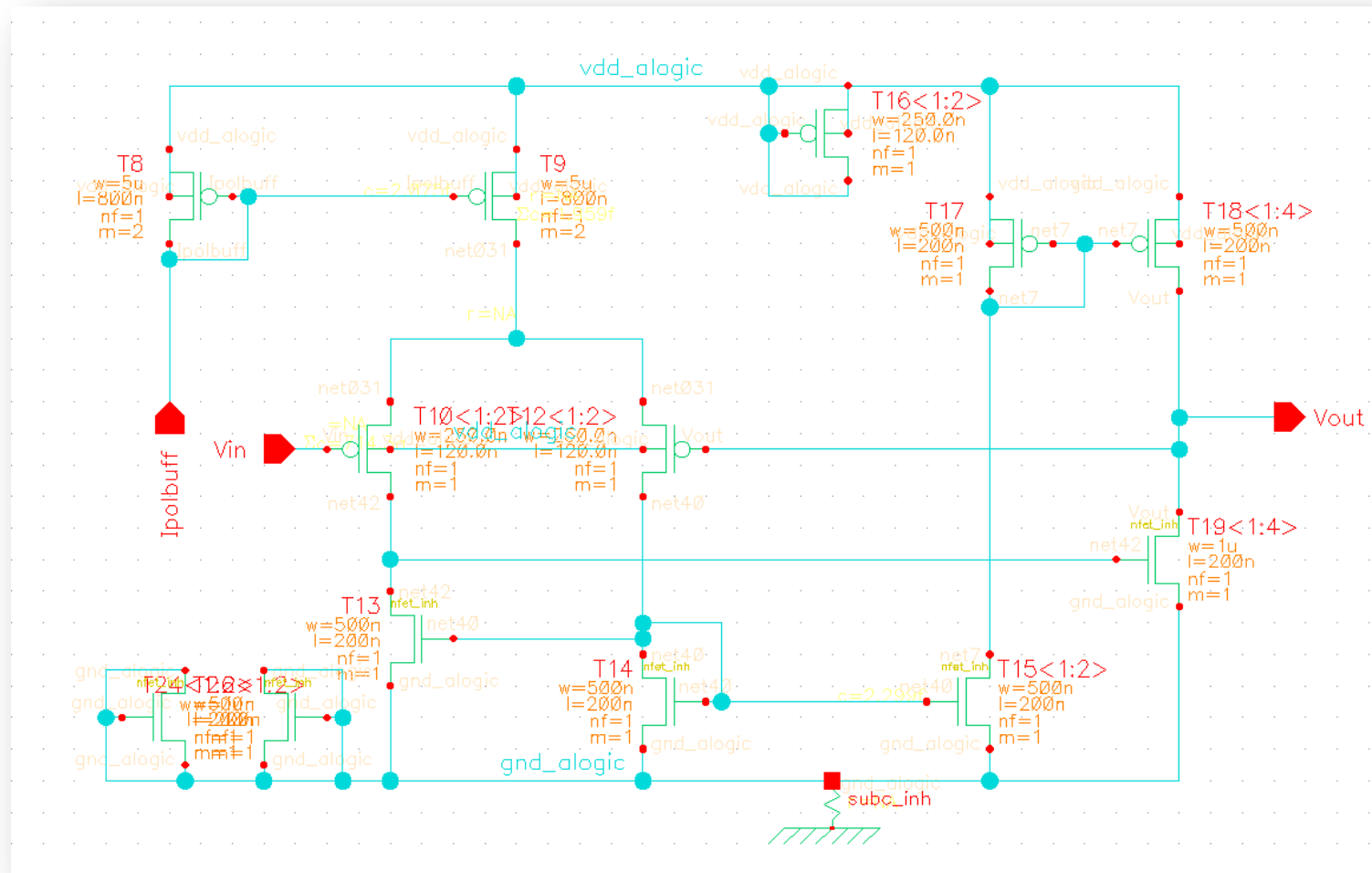

Fast buffer design

▶ Characteristics:


- 14ns buffering time < 25ns of the write cycle.
- 30 μ V of integrated noise from 1kHz to 10GHz.
- Low power: 1 μ A/buffer.

- Big offset variation due to process variation (100mV measured buffer to buffer).
- 1V linear range.




Buffer Layout

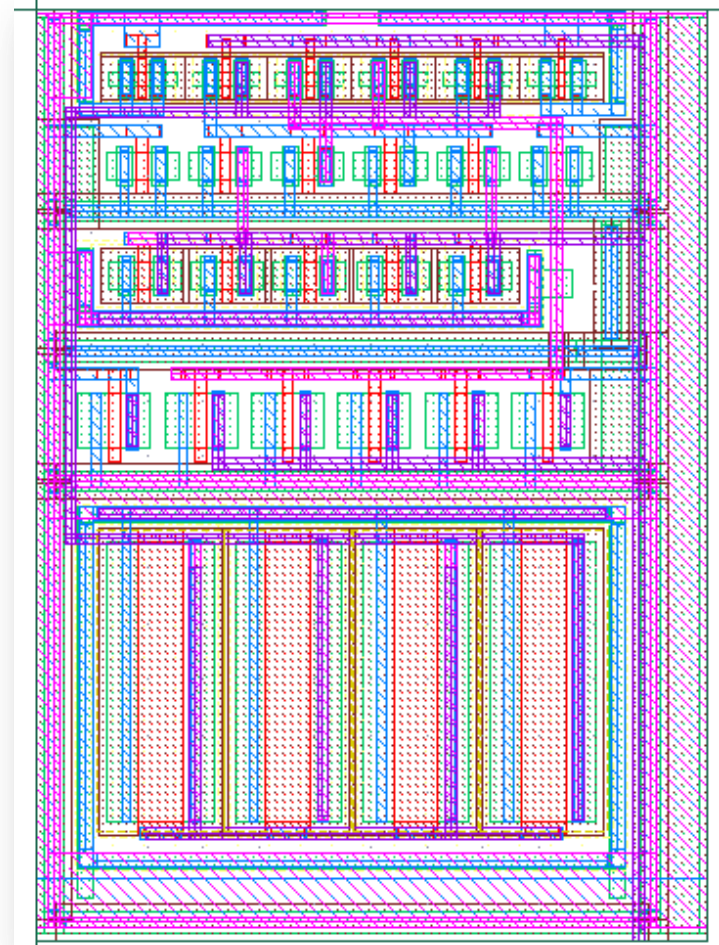- ▶ Size $12\mu\text{m} \times 16\mu\text{m}$.
- ▶ Internal current source.
- ▶ Copy of the buffer previously implemented.






1V Linear Dynamic Range

 




Buffer – Rise time

 


Buffer Noise

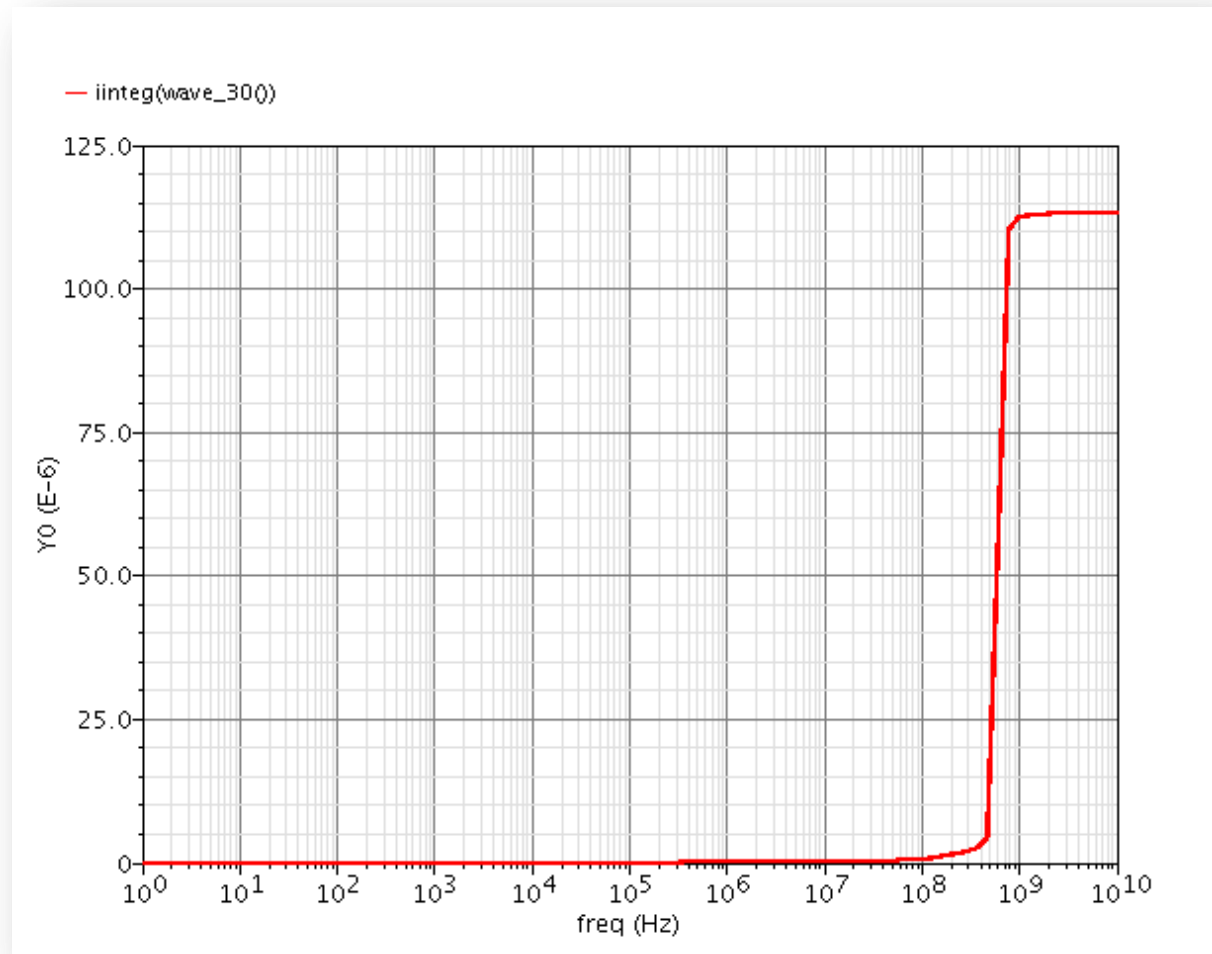Total integrated
noise = $120\mu\text{V}$.





Sampling with buffer

 



Sampling without buffer

