

Design Review



PSEC3 8-2-2010

Trigger


- structure
- triggering scheme

Eric Oberla

schematic/layout

 
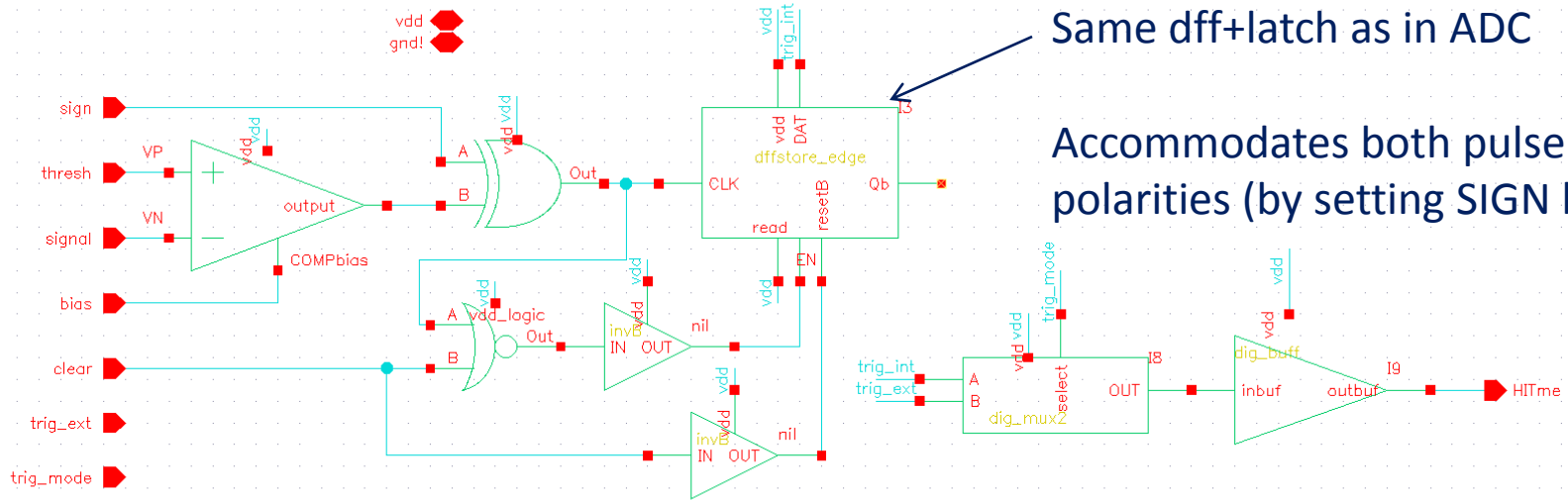


comparator

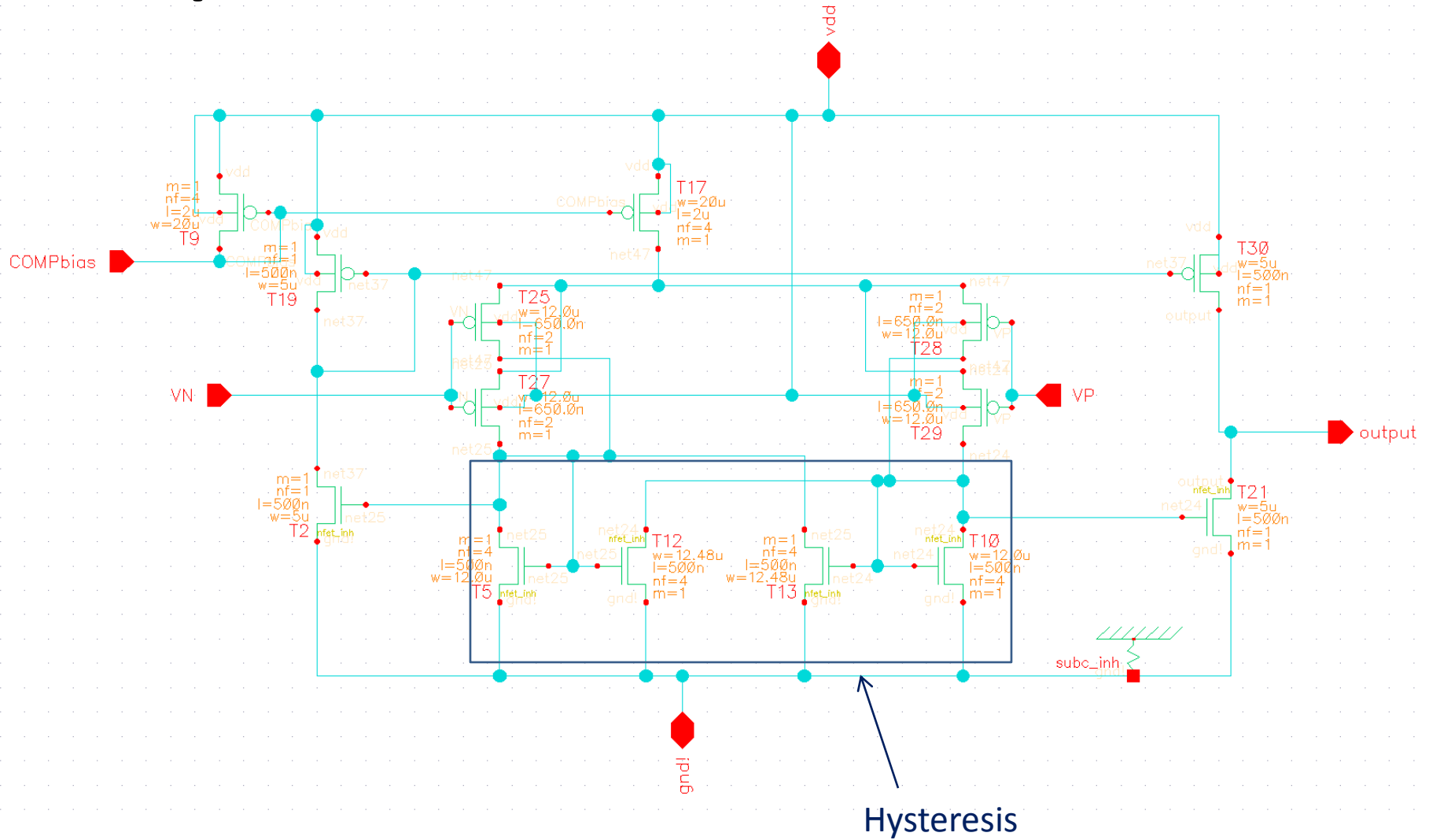

comparator

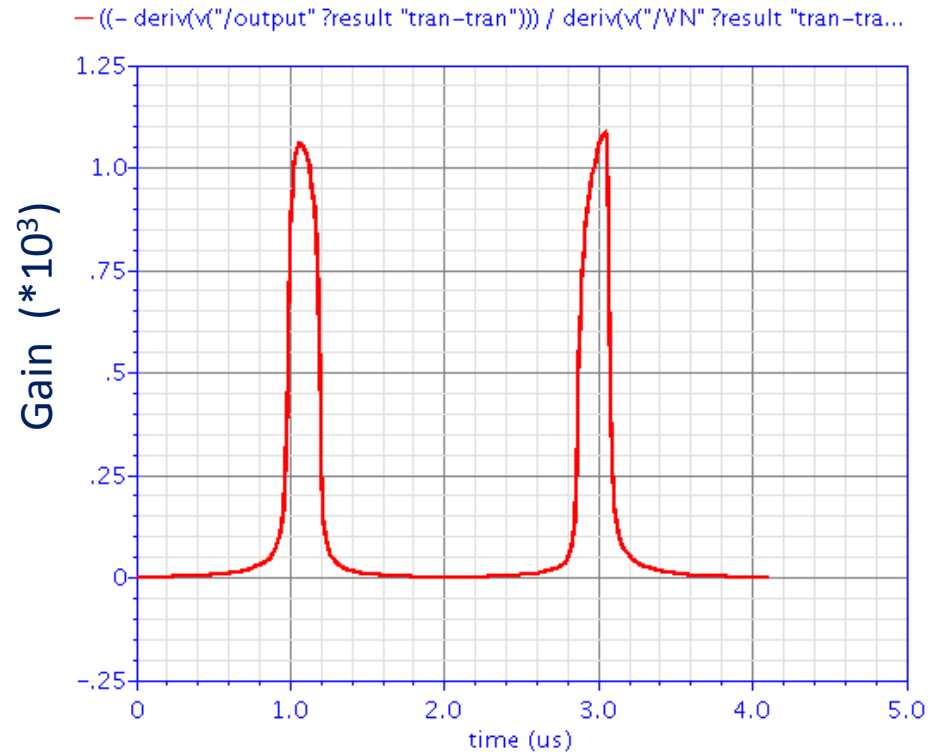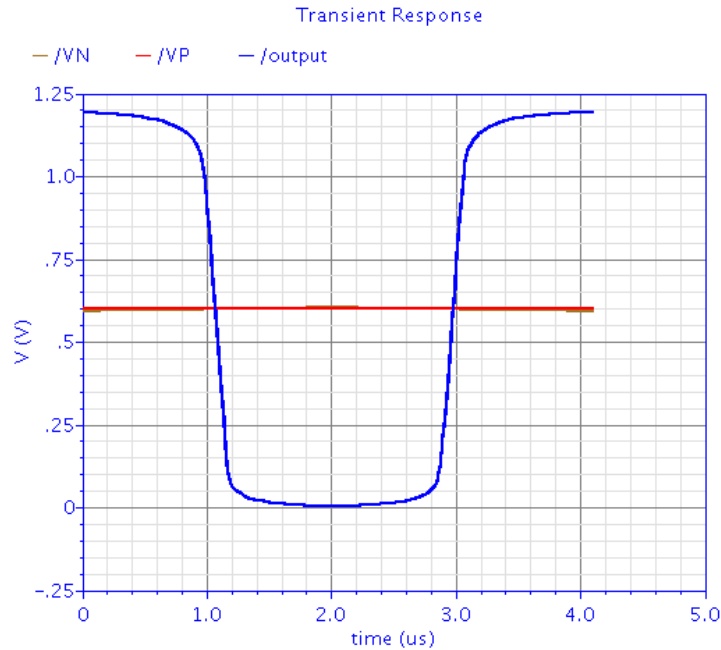Gain = 1000 (nearly independent of bias 20-100 μA)



Triggering scheme

- Each analog input discriminator has a dedicated output pad
- There is also a triggerOR output. This is the OR of the five trigger signals.
 - This will be useful when outfitting an 80 channel detector, reducing the number of traces by a factor of 5 (if we only care about trigger/chip rather than trigger/channel).
- Individual trigger and/or triggerOR output(s) sent to FPGA, which resends common trigger that freezes all channels. This must be done within 25 ns, before sampling cells are overwritten.
- Channel 6 is a dedicated timing channel, allowing location of triggered event
- Readout all channels, or only those of interest

simulation (post-layout)

