

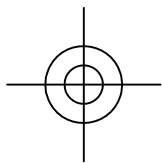


FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_1:Top: Signal\_1


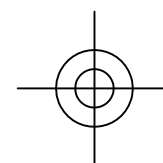


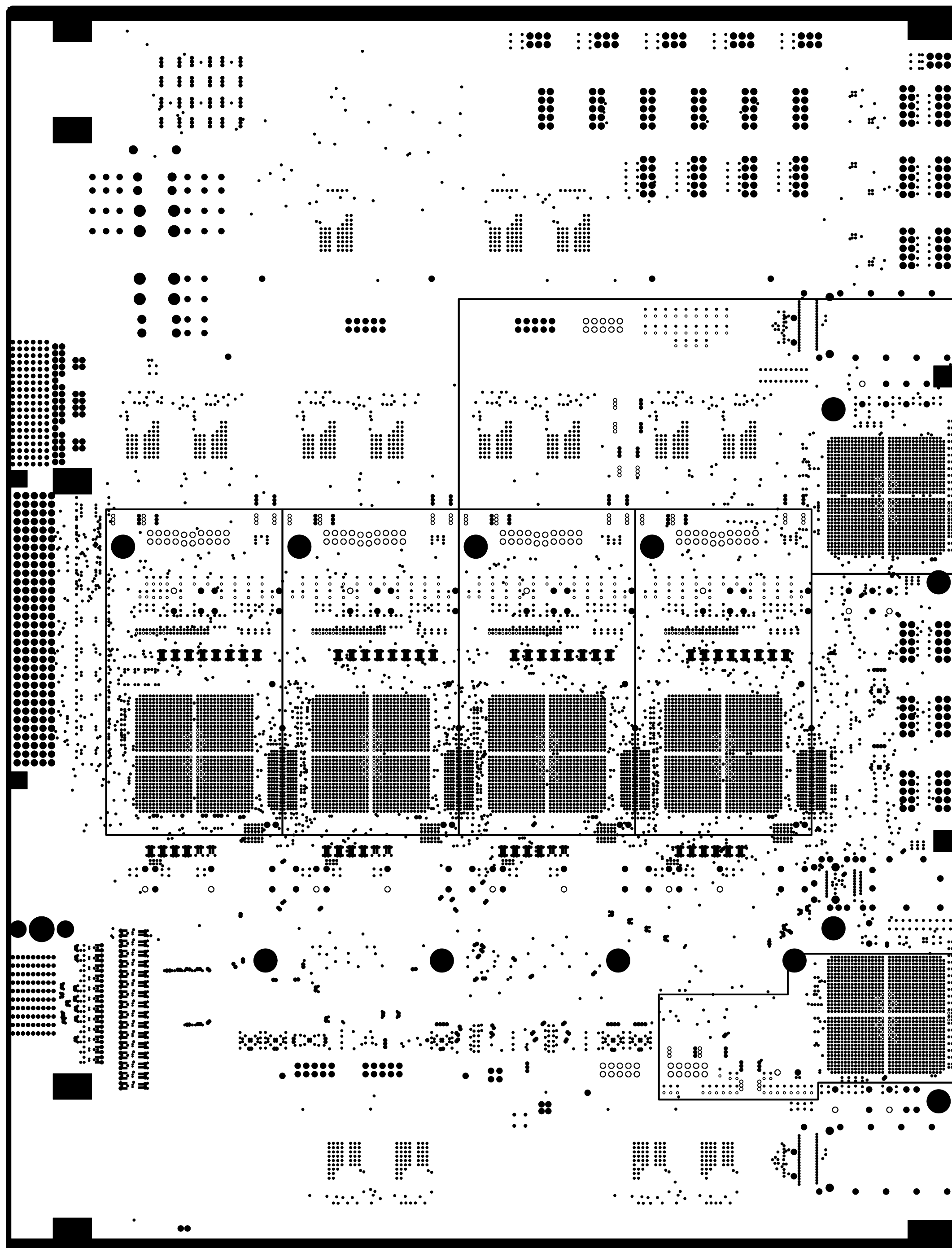

FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

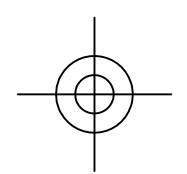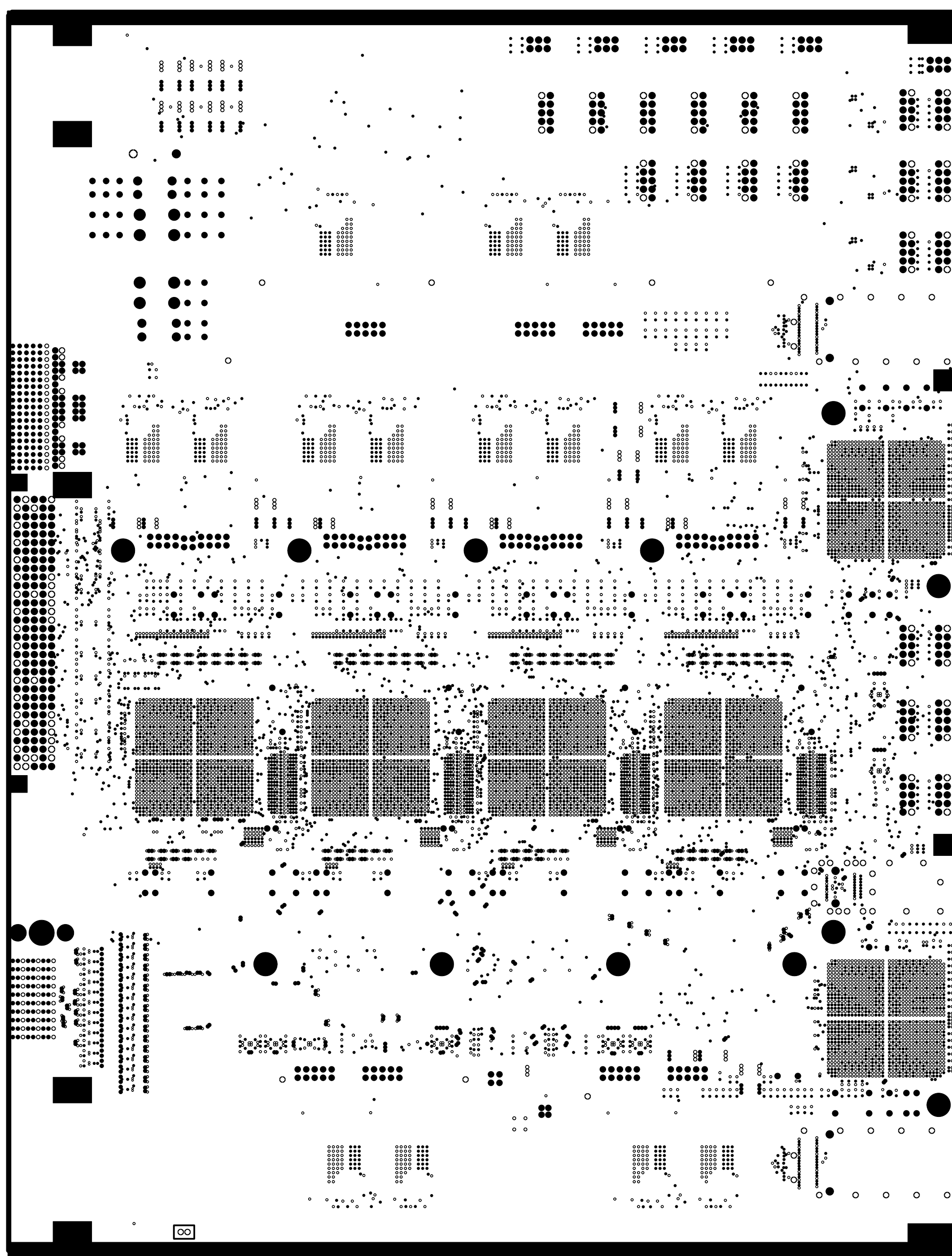Artwork\_2: 1.15V, VCC\_1.1V\_1,2,3,4,5,6






FTK Rear VME Test Card  
March 25, 2013  
8:49 am

Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_3: Ground1

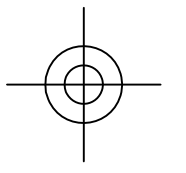
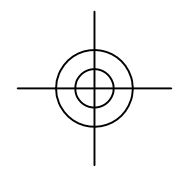


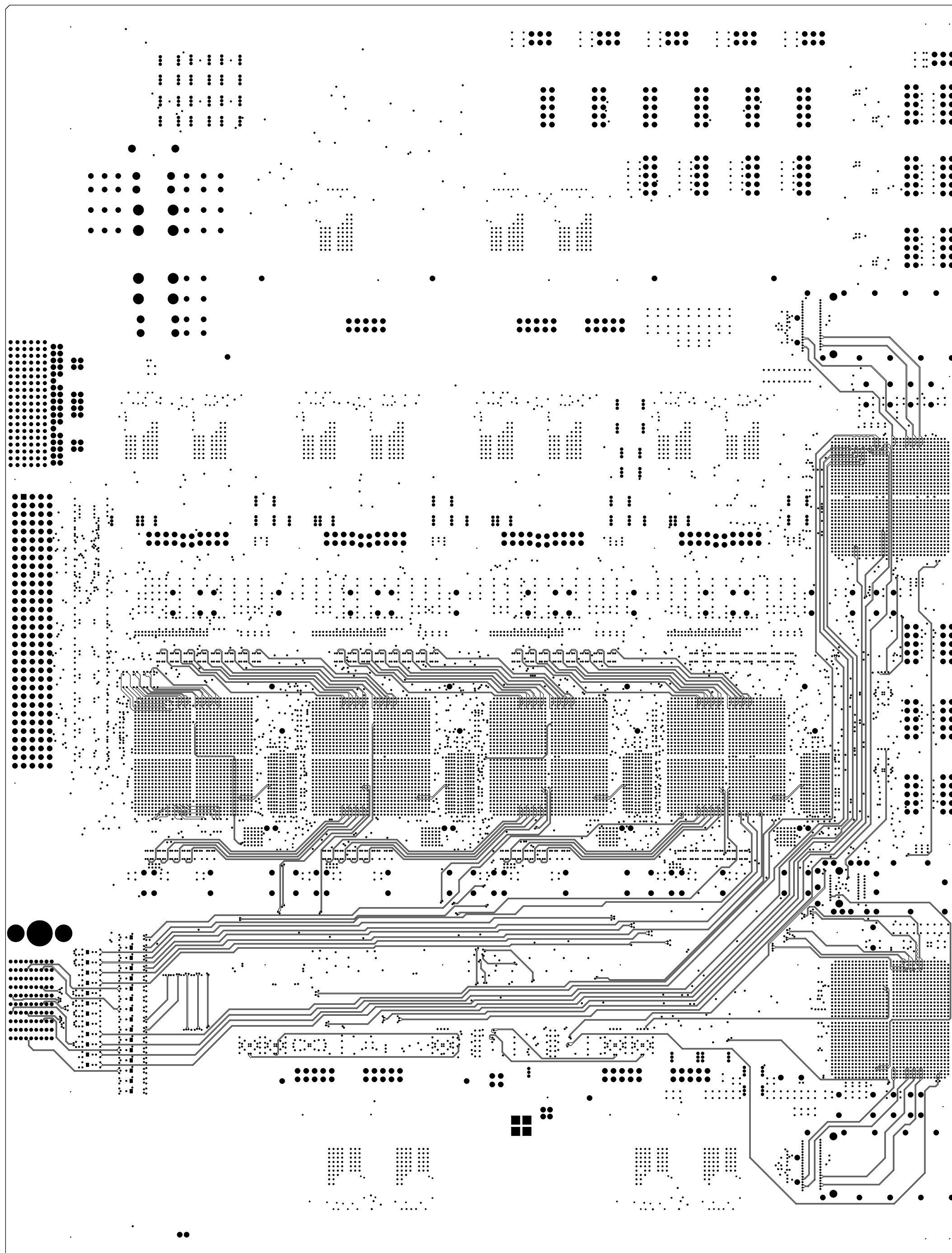

FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_4: Signal\_2

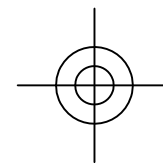
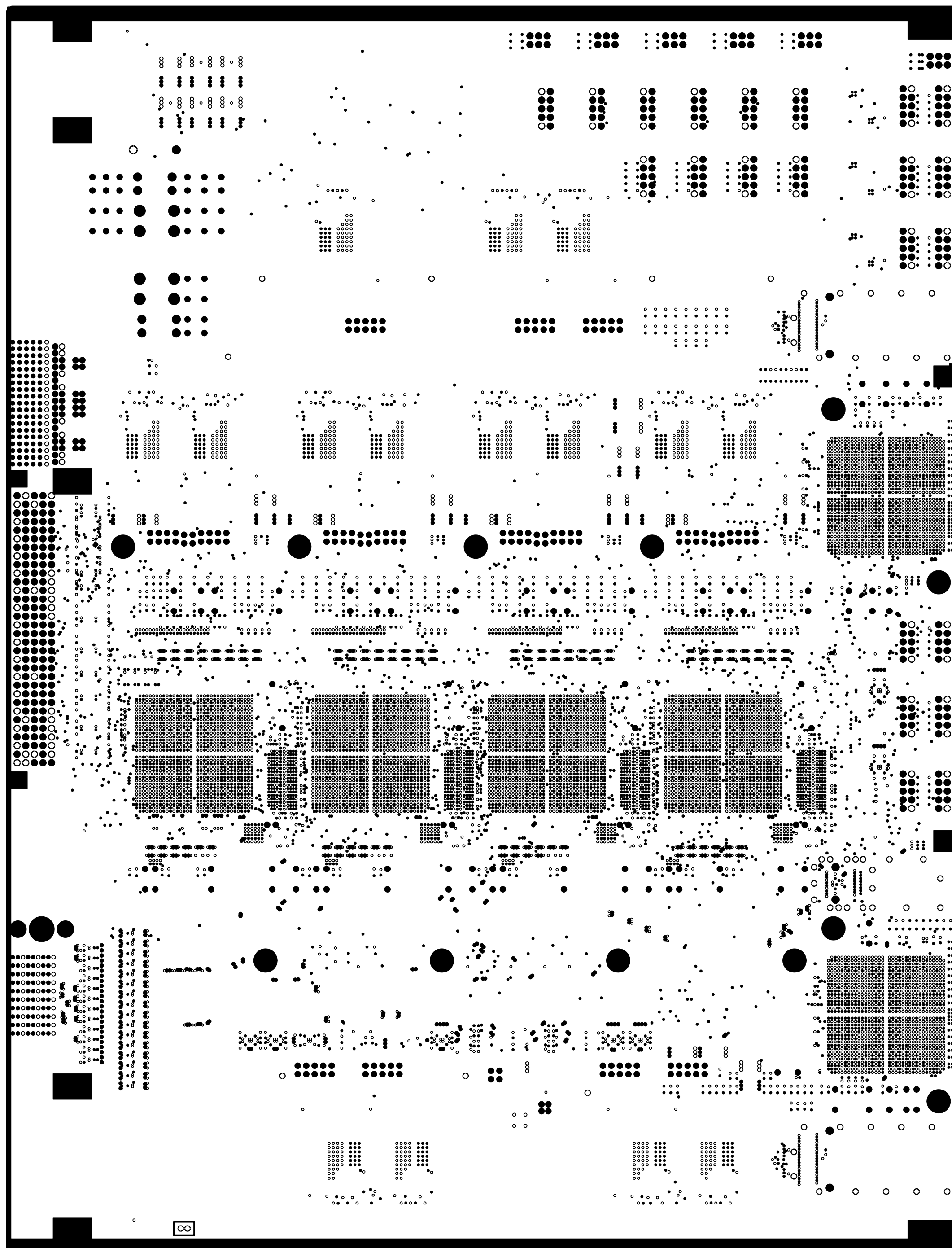


FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am




Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

Artwork\_5: Ground2

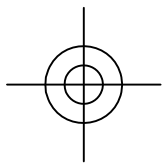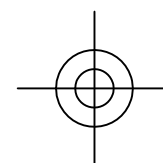





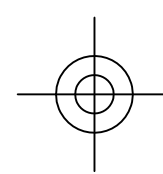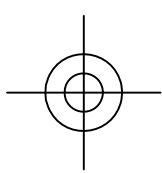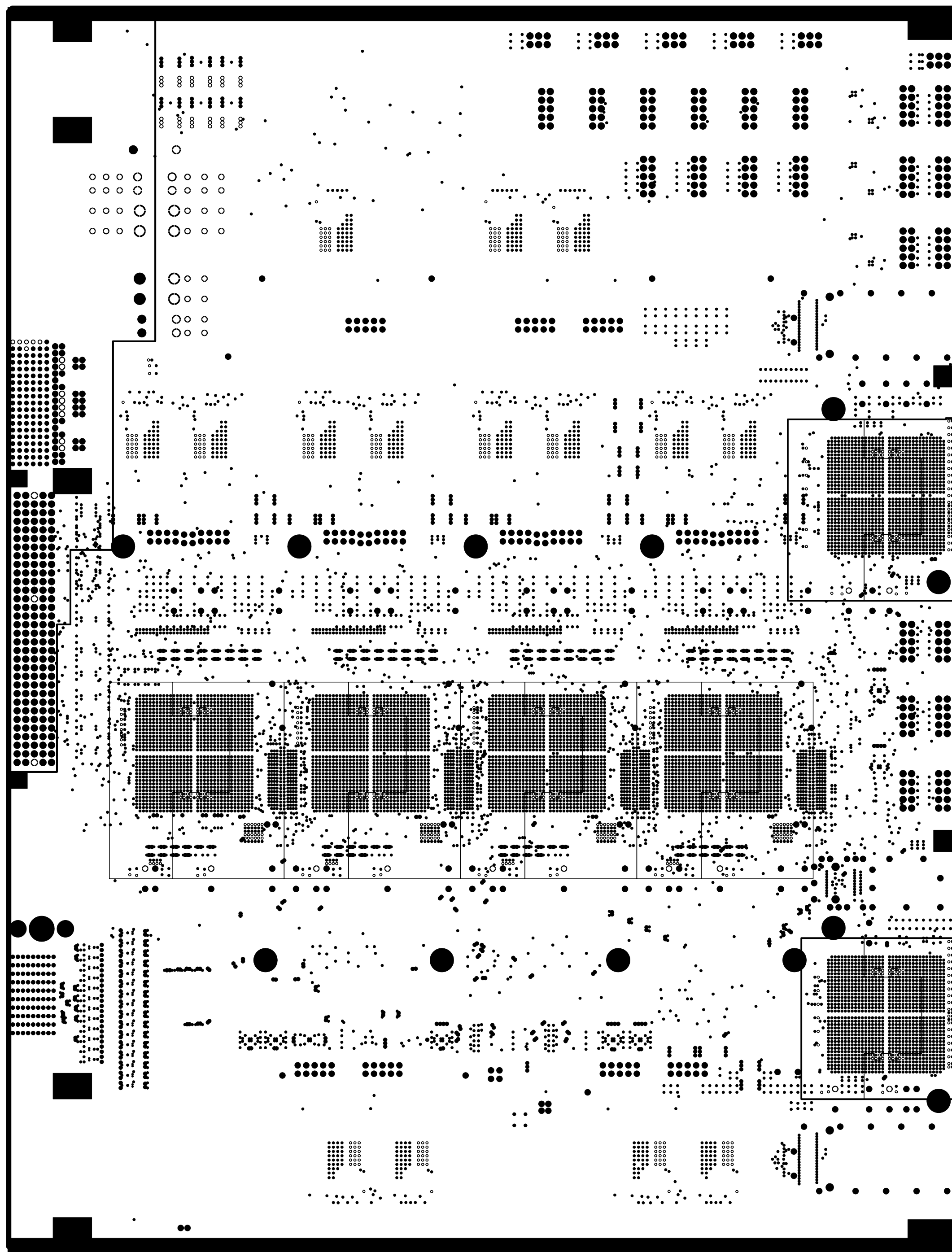


FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

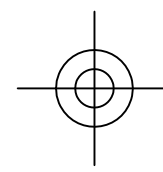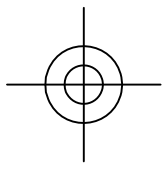Artwork\_6: +5Vin,+5Vcc, T\_GXB\_1,...,6, LR\_GXB\_1,...,6




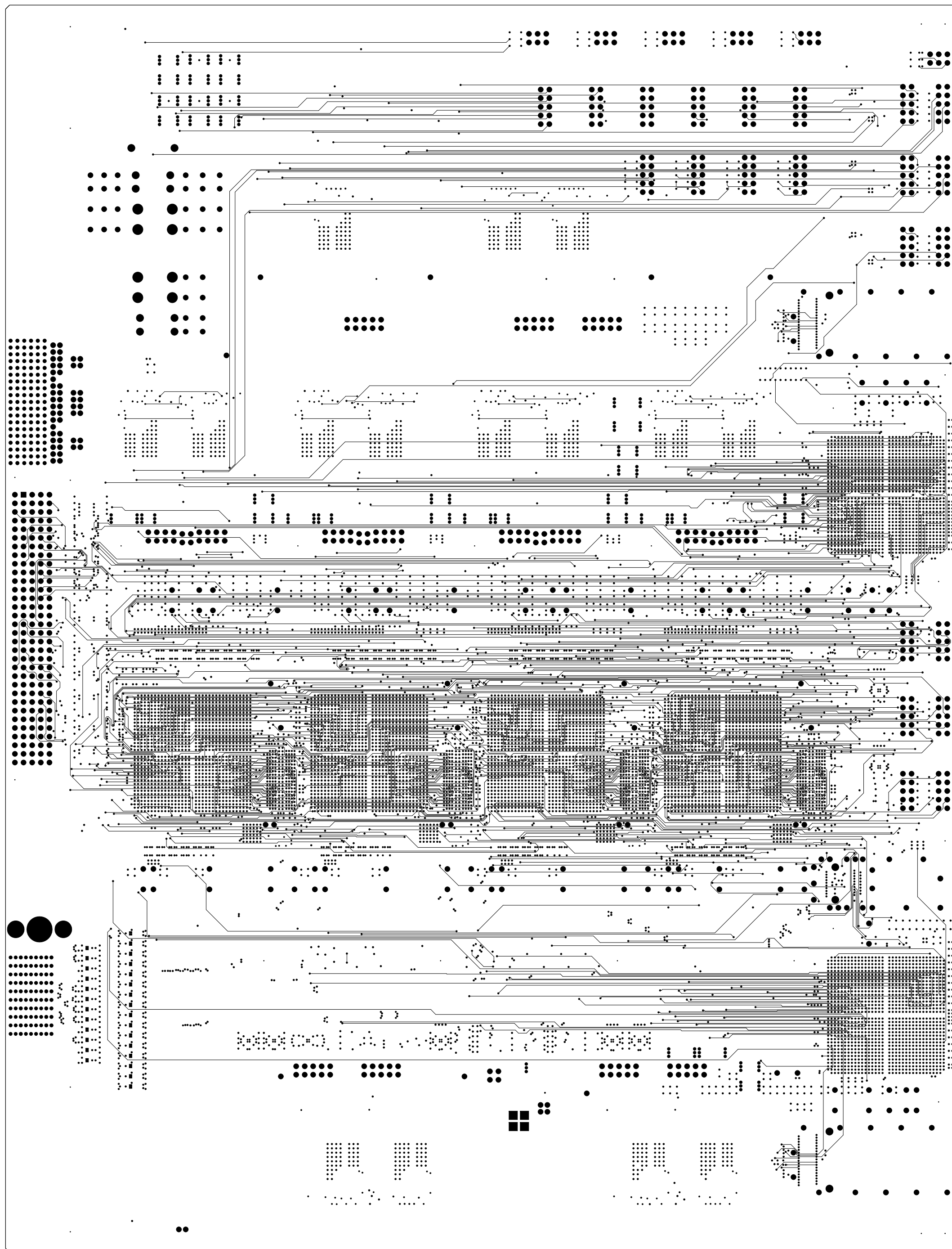

FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_7: Signal\_3



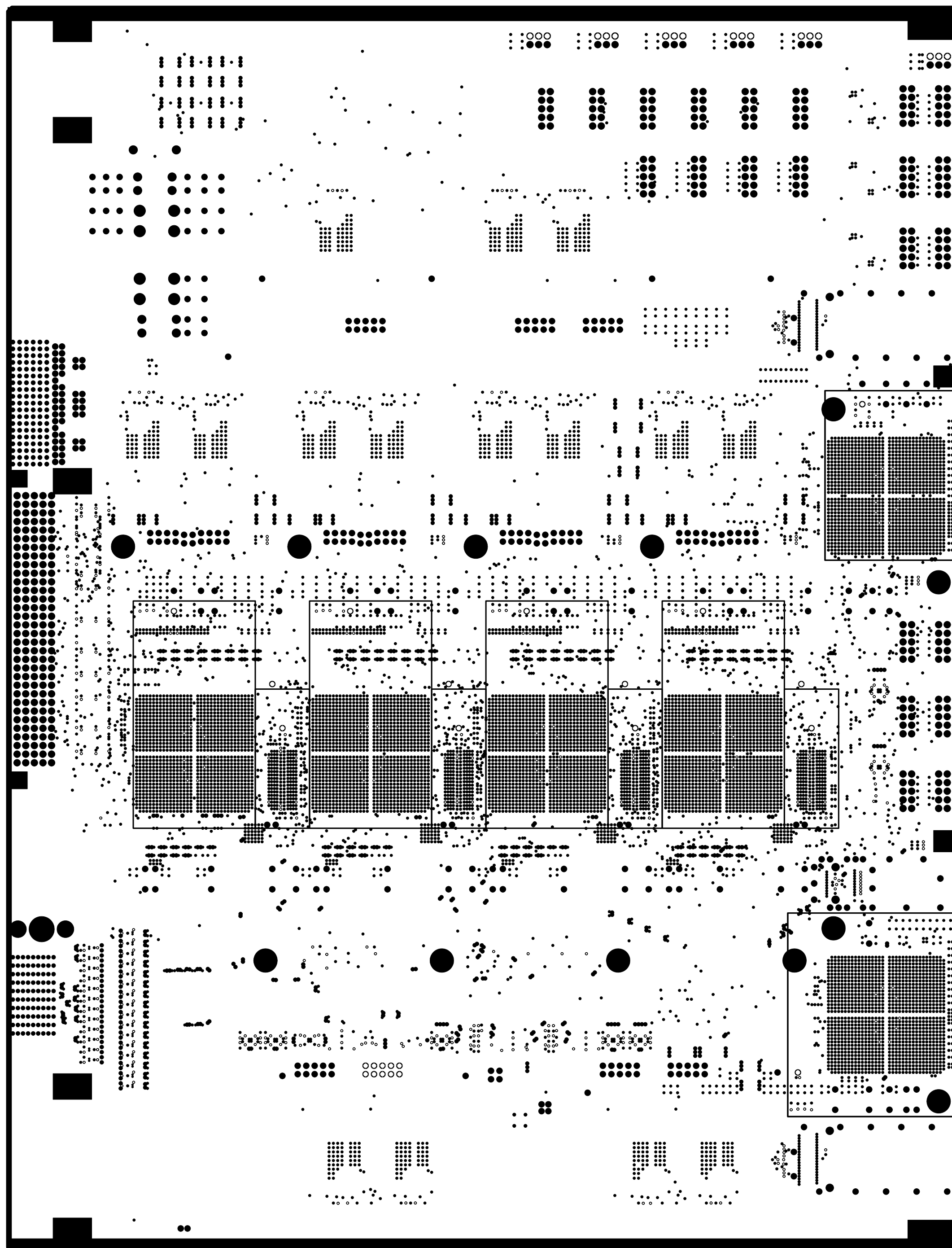


FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

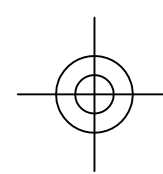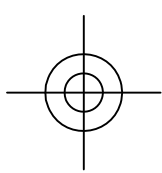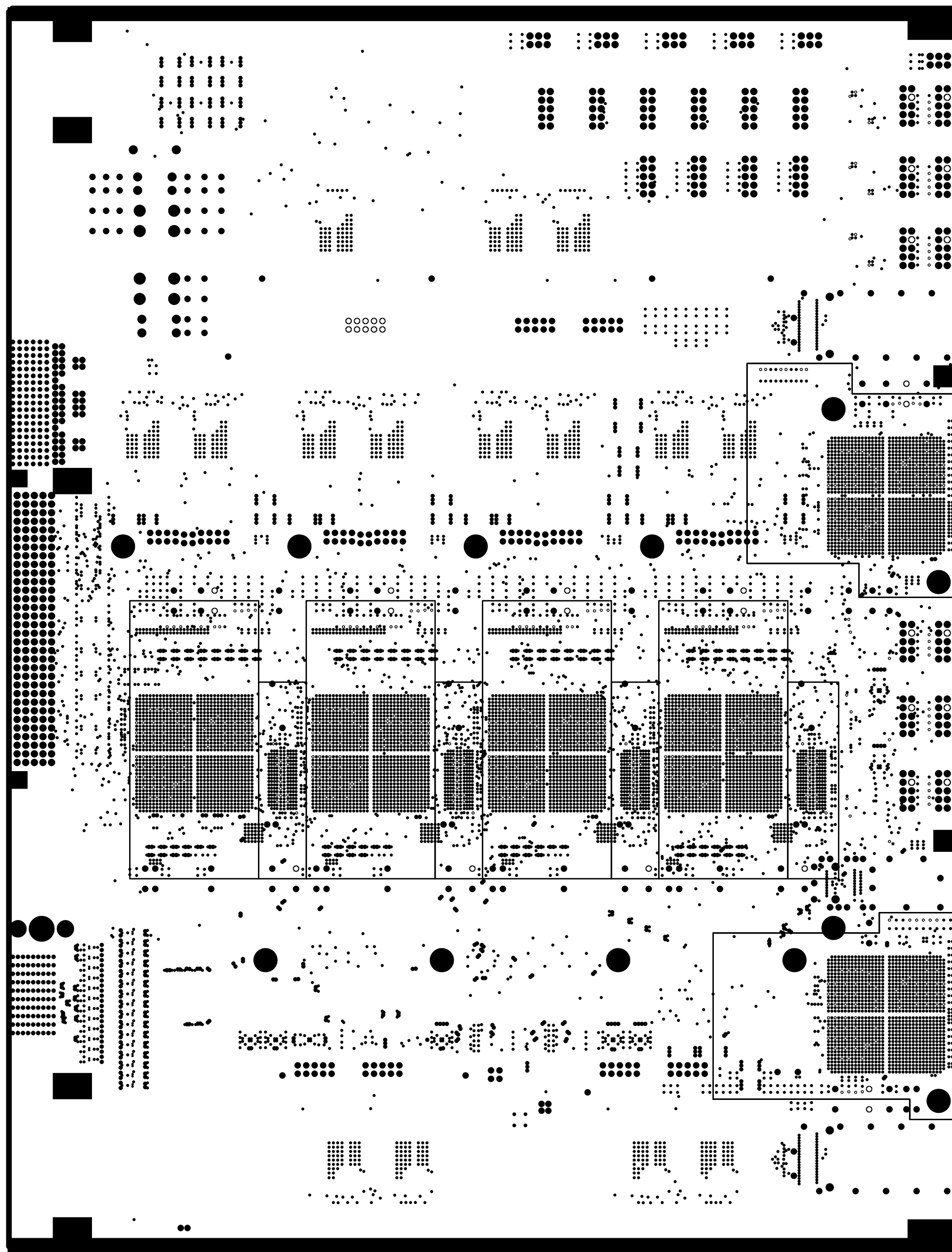Artwork\_8: 3.3V, VCCP\_1.1V\_1,2,3,4,5,6, VTT\_0.9V\_1,2,3,4








FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

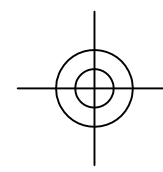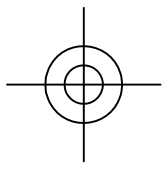Artwork\_9: 3.0V, V10\_3.0V\_1,2,3,4,5,6, VDDQ\_1.8V\_1,2,3,4




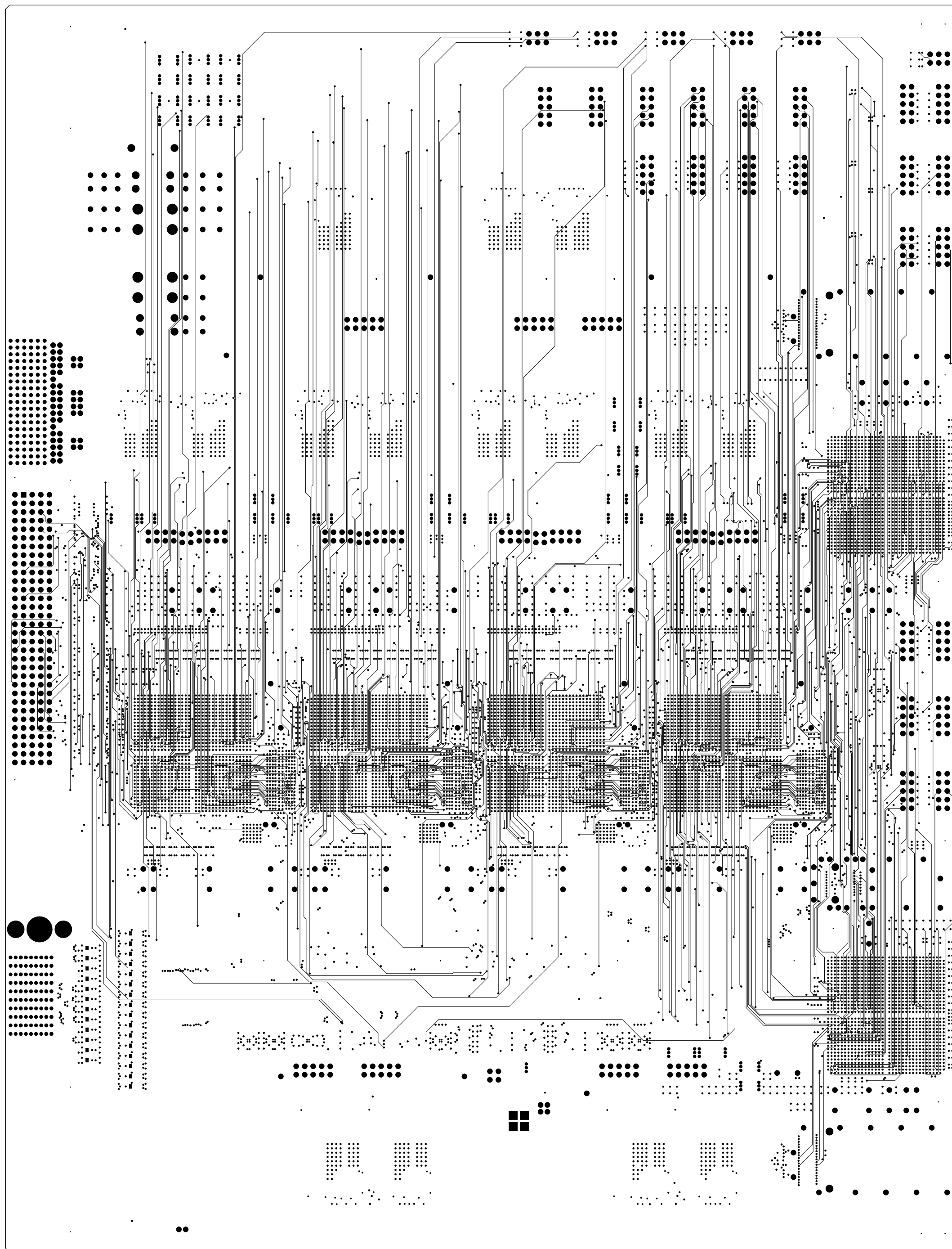

FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A


Artwork\_10: Signal\_4

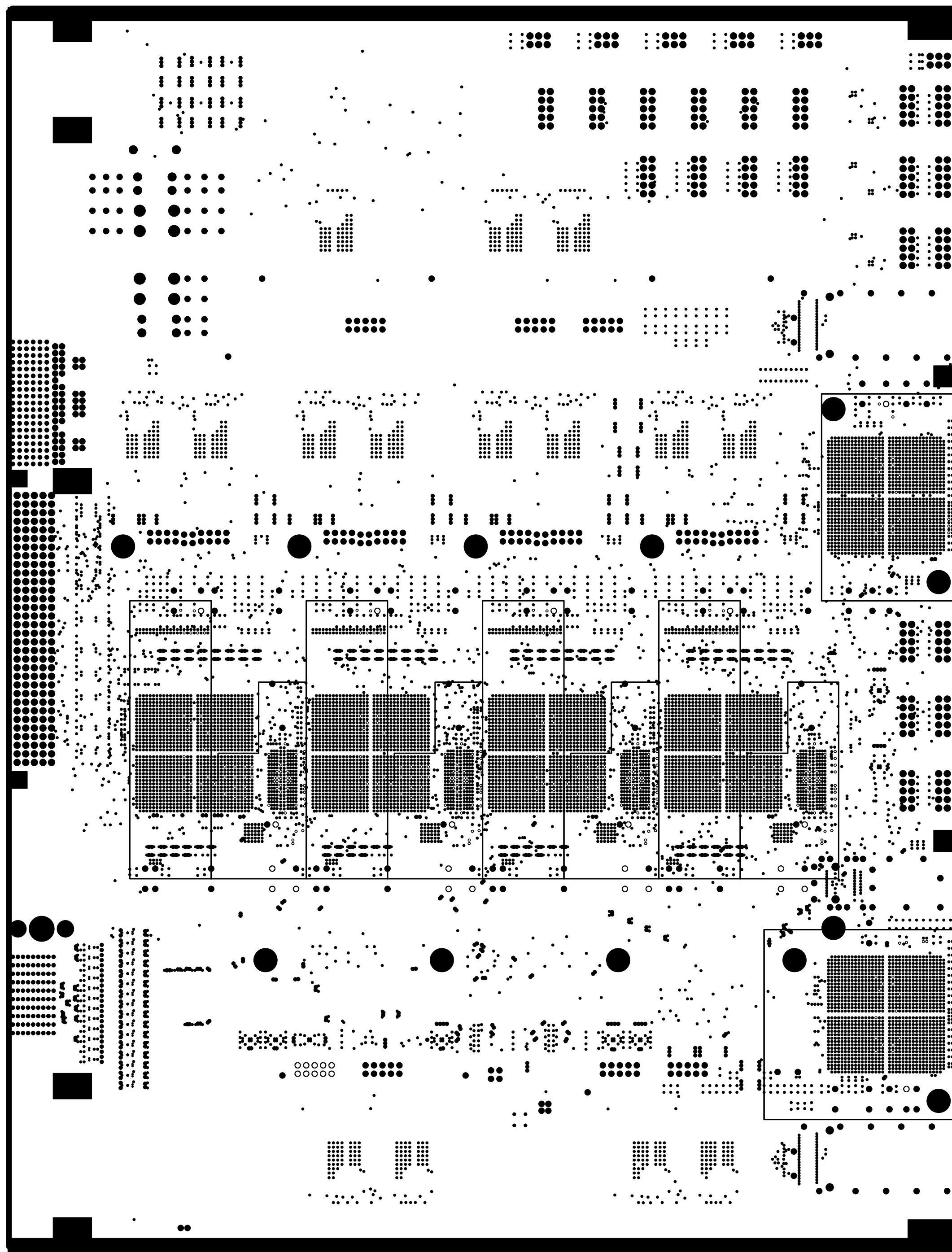

FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

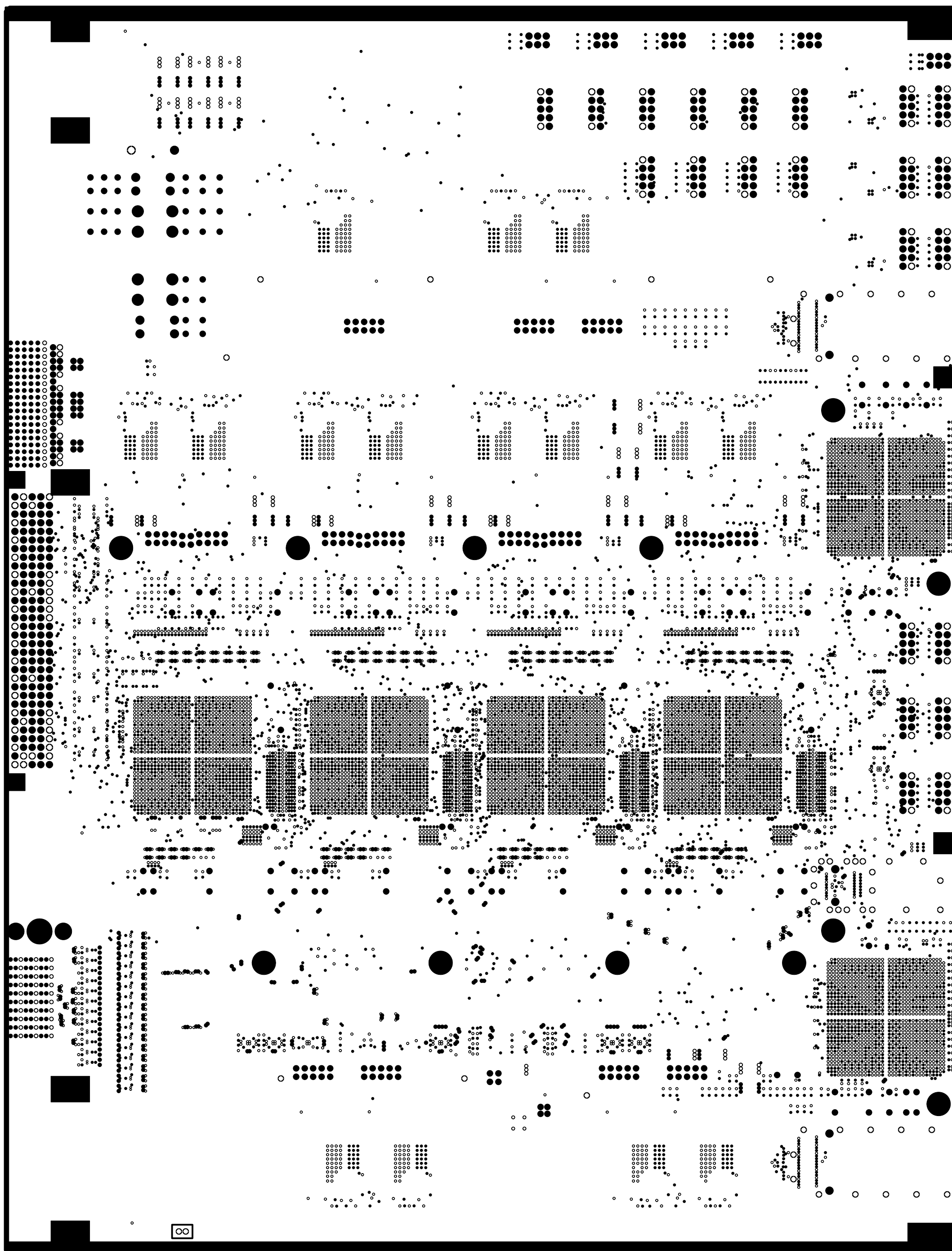Artwork\_11: 1.8V, VAUX\_2.5V\_1,2,3,4,5,6, V10\_1.8V\_1,2,3,4




FTK Rear VME Test Card  
March 25, 2013  
8:49 am

Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_12: Ground3



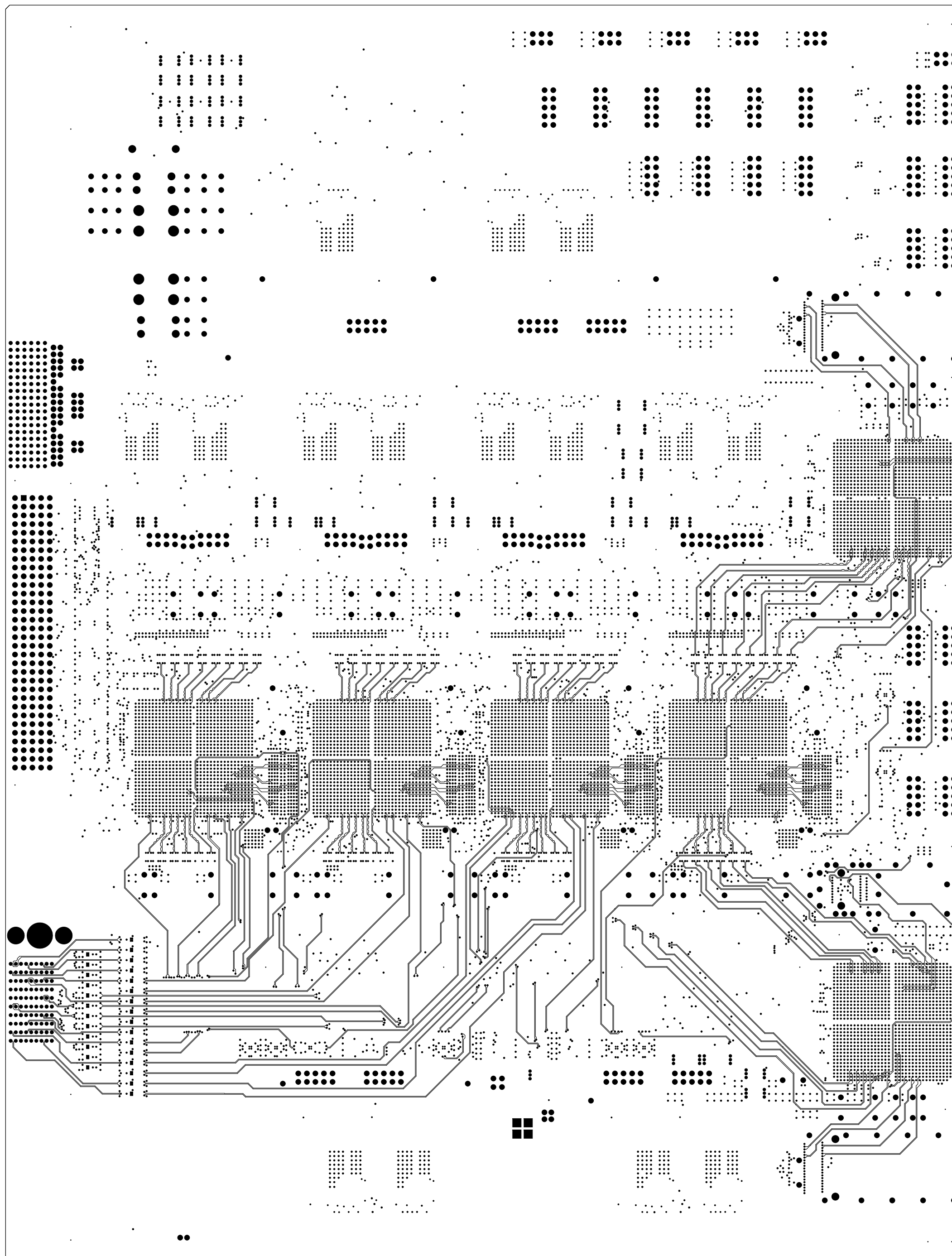


FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_13: Signal\_6



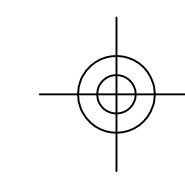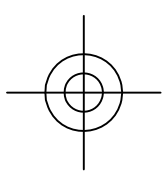
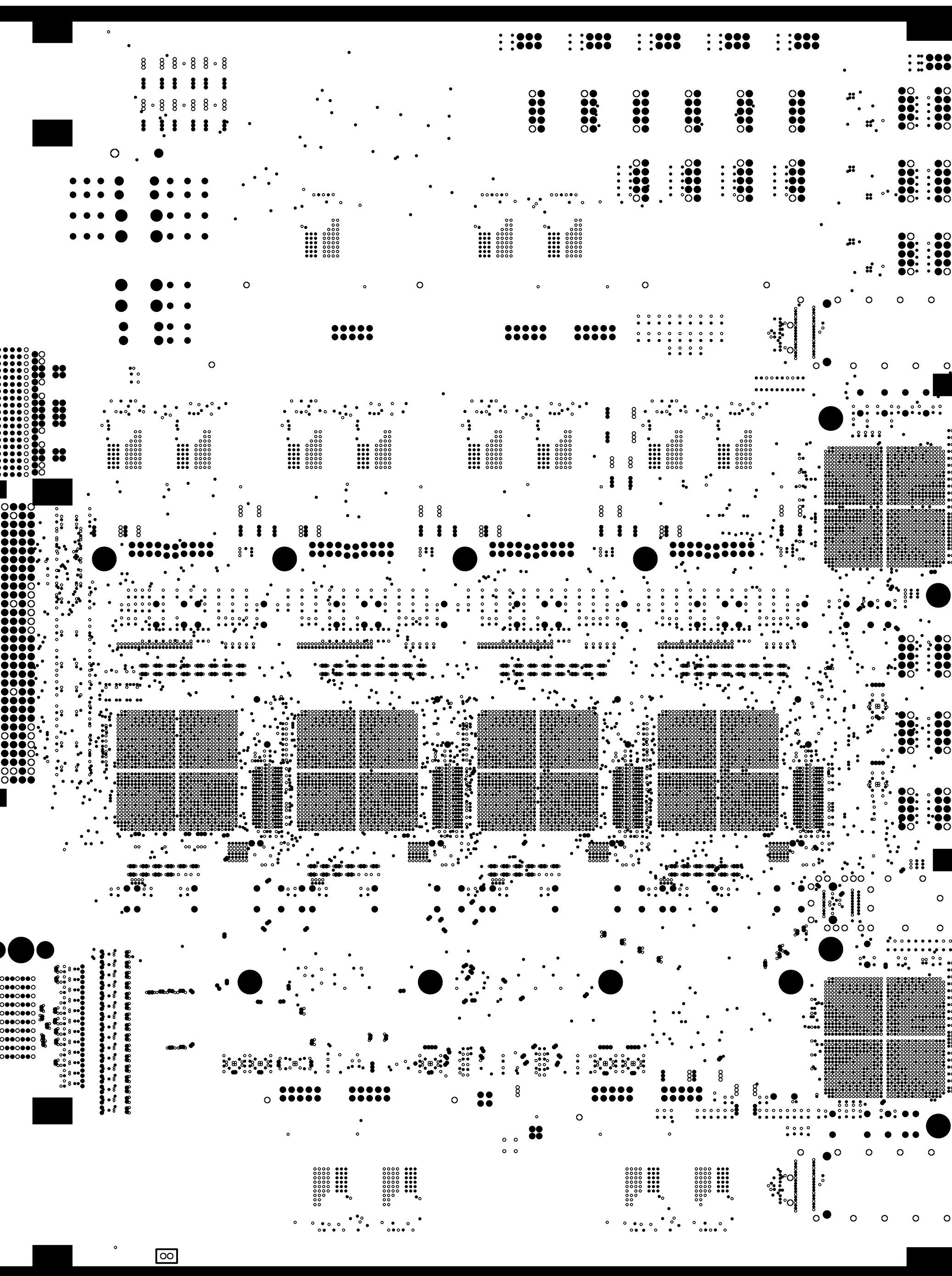





FTK Rear VME Test Card  
March 25, 2013  
8:49 am

Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_14: Ground4

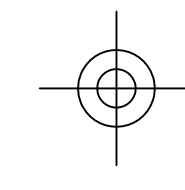
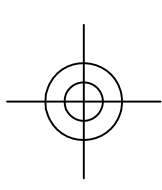


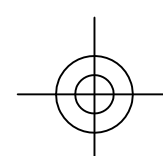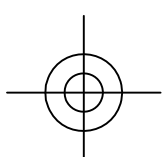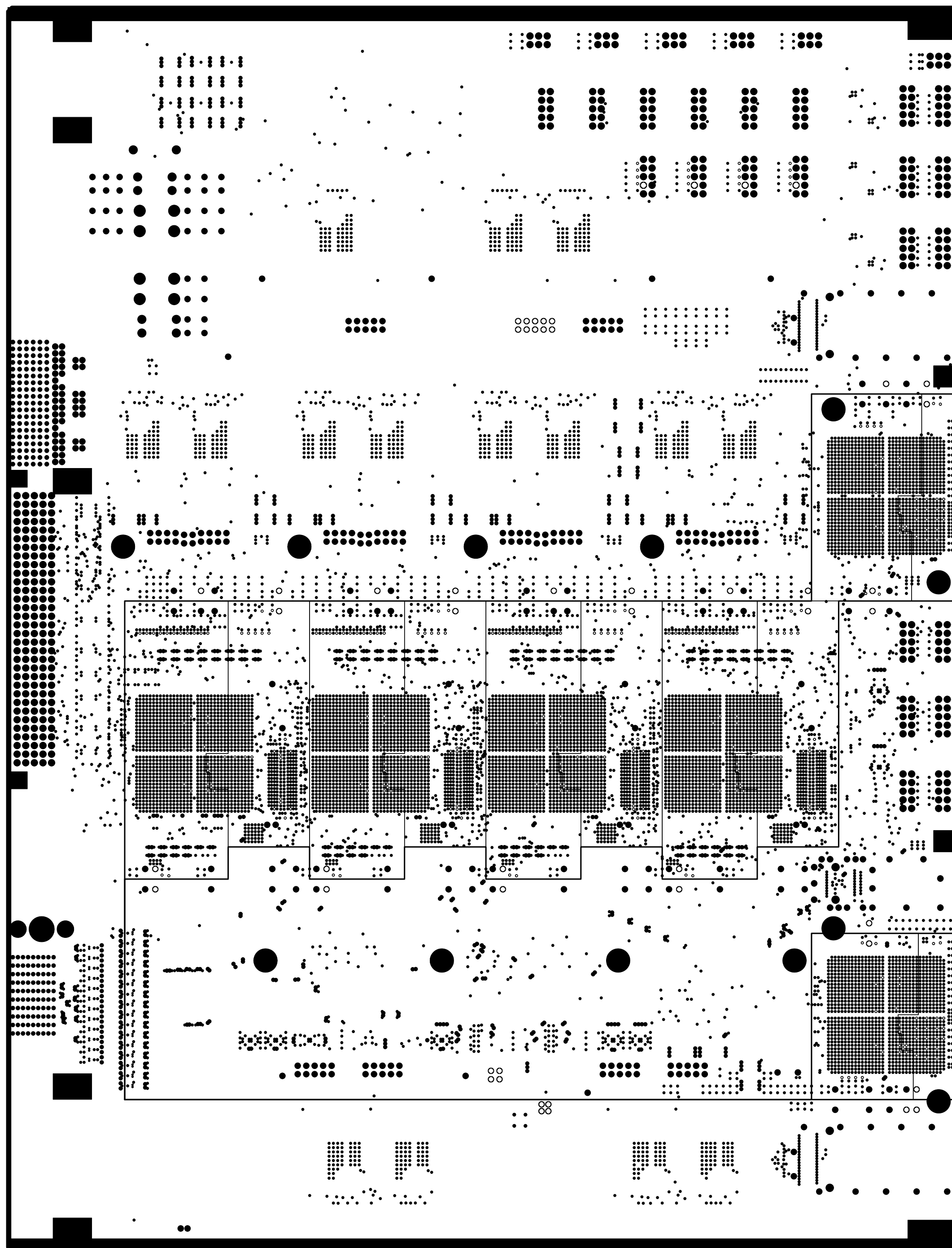


FTK Rear VME Test Card  
March 25, 2013  
8:49 am  
Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

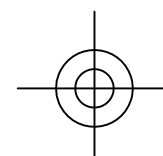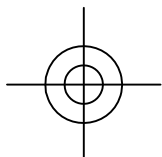Artwork\_15: 2.5V, 1.5V, V10\_2.5V\_1,2,3,4,5,6, H\_GXB\_1.5V\_1,2,3,4,5,6



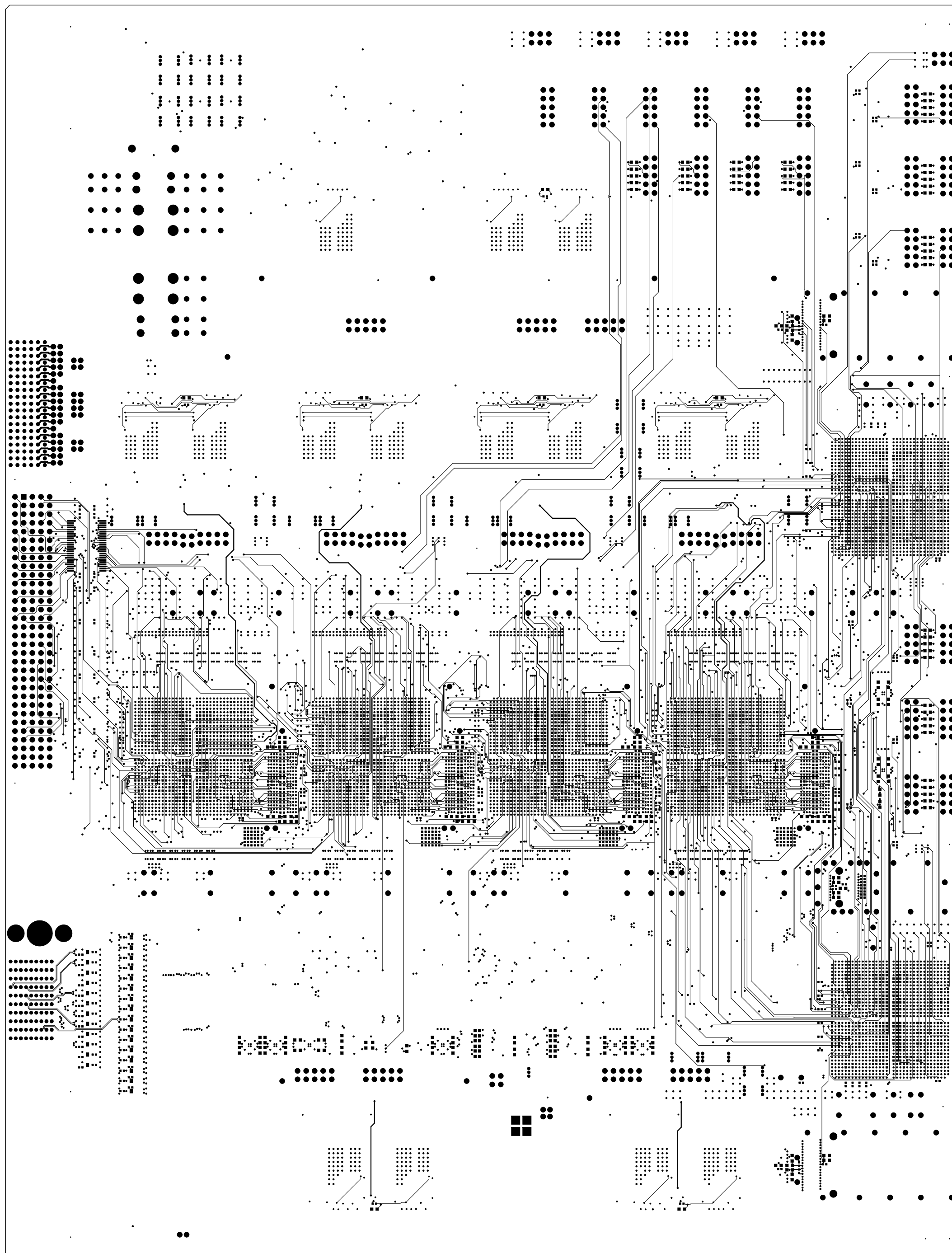



FTK Rear VME Test Card  
March 25, 2013  
8:49 am

Mircea Bogdan  
Electronics Design Group  
University Of Chicago

Sch. Draw 2808 Rev A  
Spc. Draw 2809 Rev A  
Asy. Draw 2810 Rev A

Artwork\_16: Signal\_6, Bottom




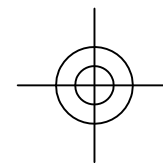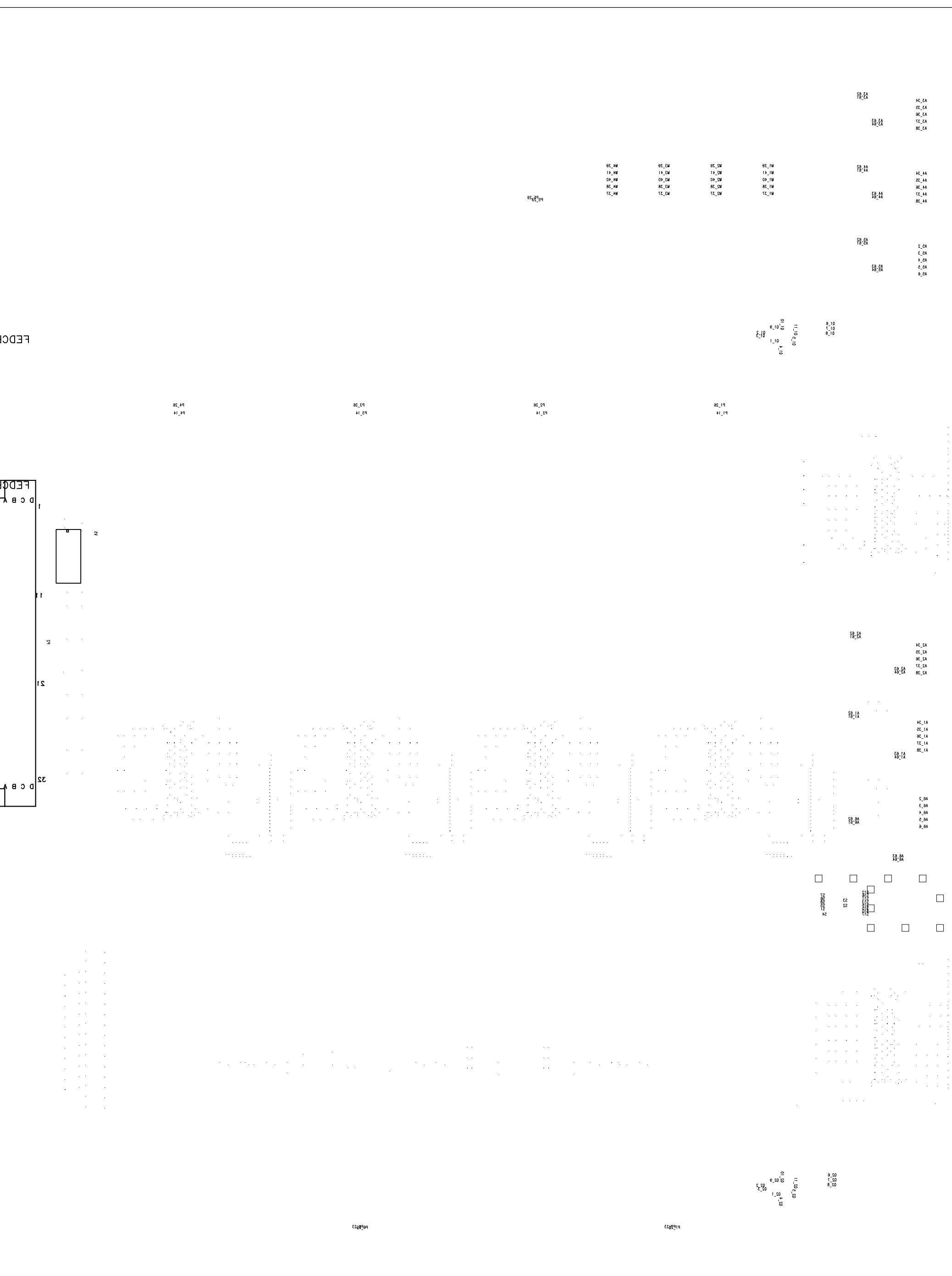



FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

Artwork\_18: Bottom Silkscreen

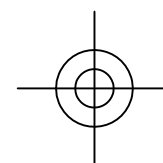



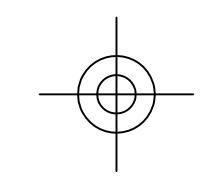
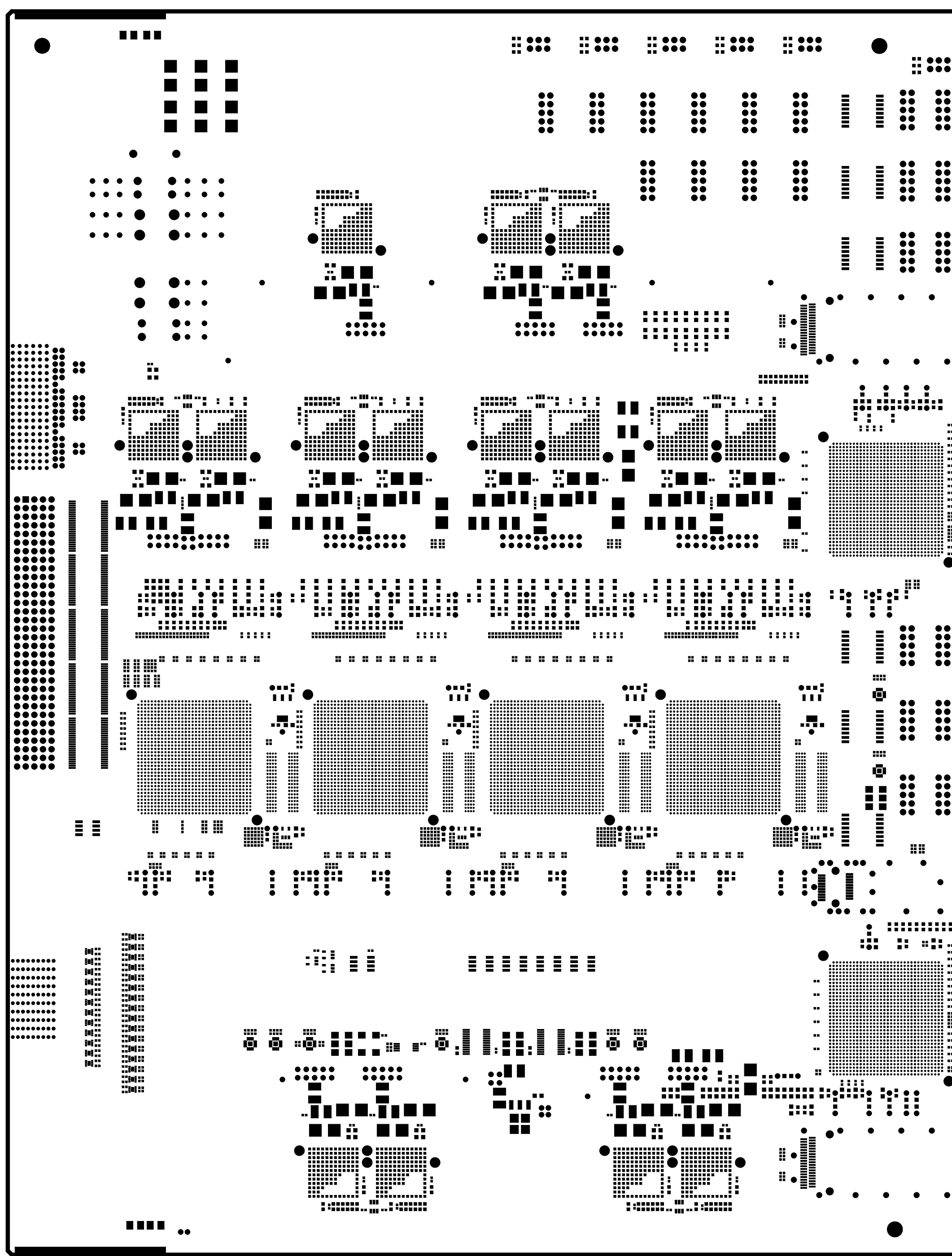




FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am

Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

Artwork\_19: Top Soldermask


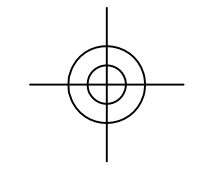
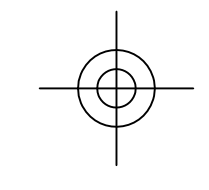


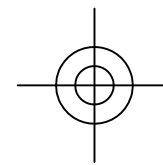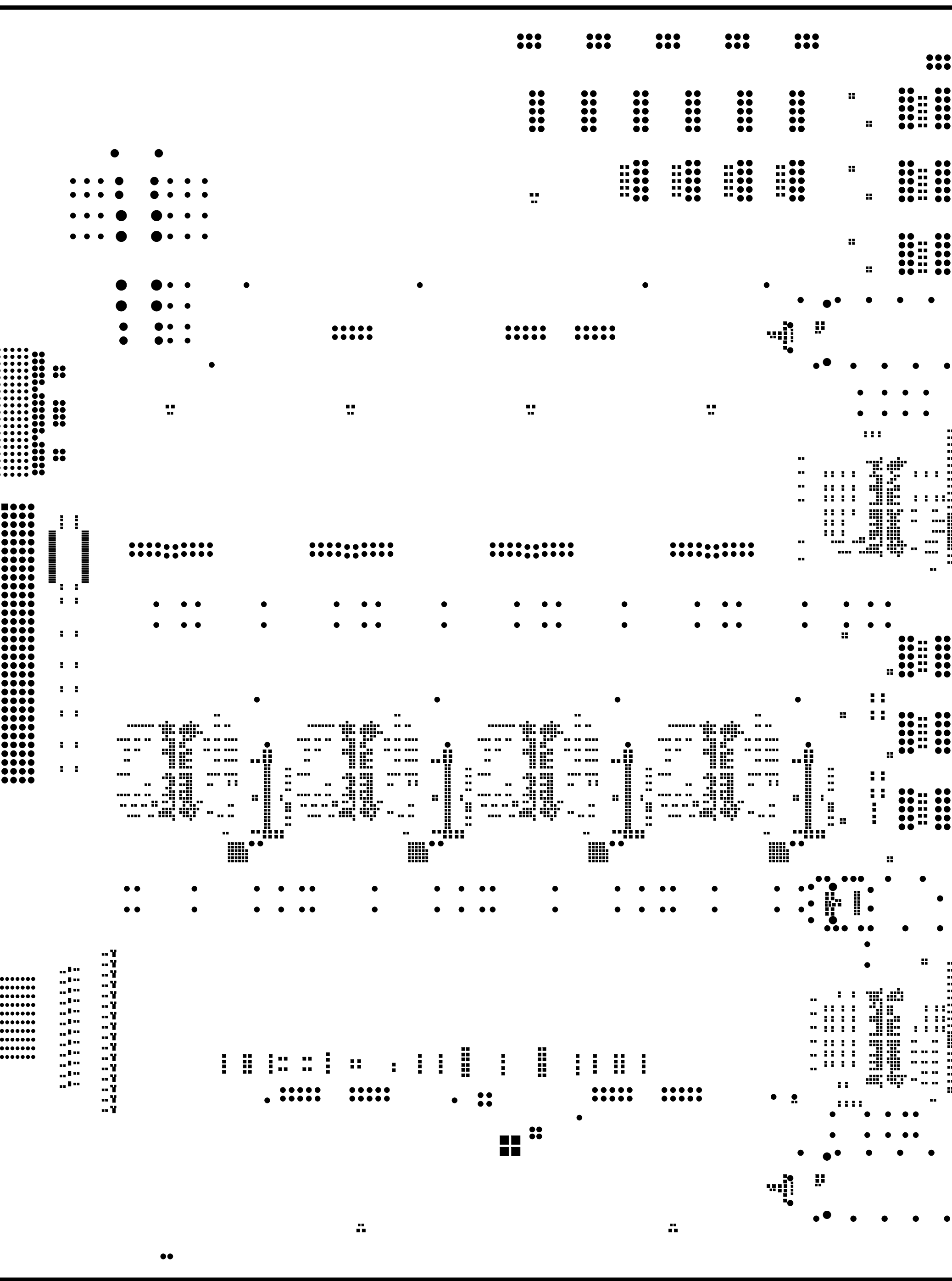


FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

Artwork\_20: Bottom Soldermask

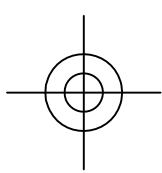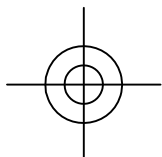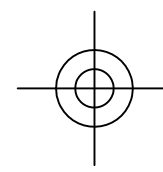


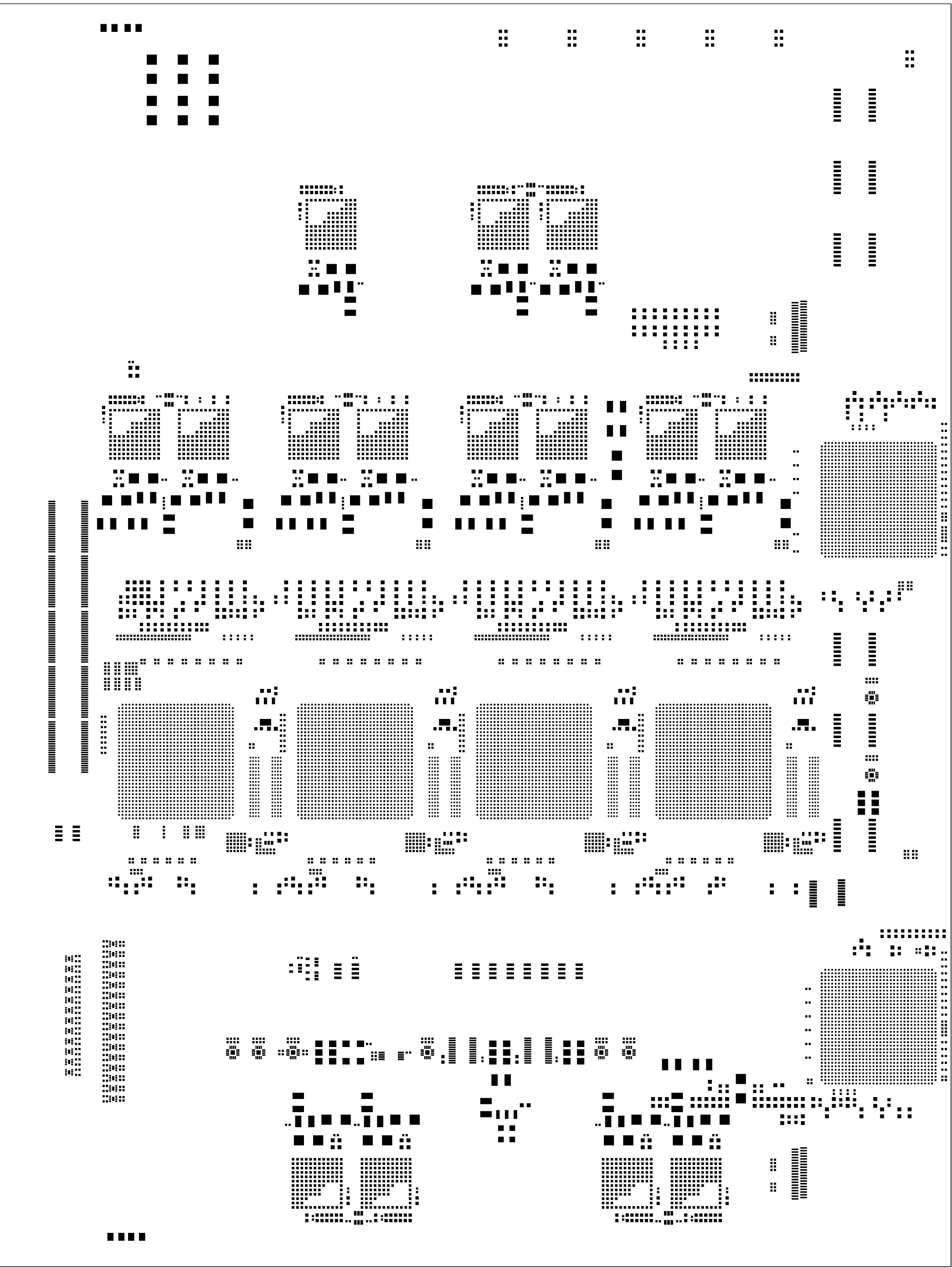

FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

Artwork\_21: Top Pastemask

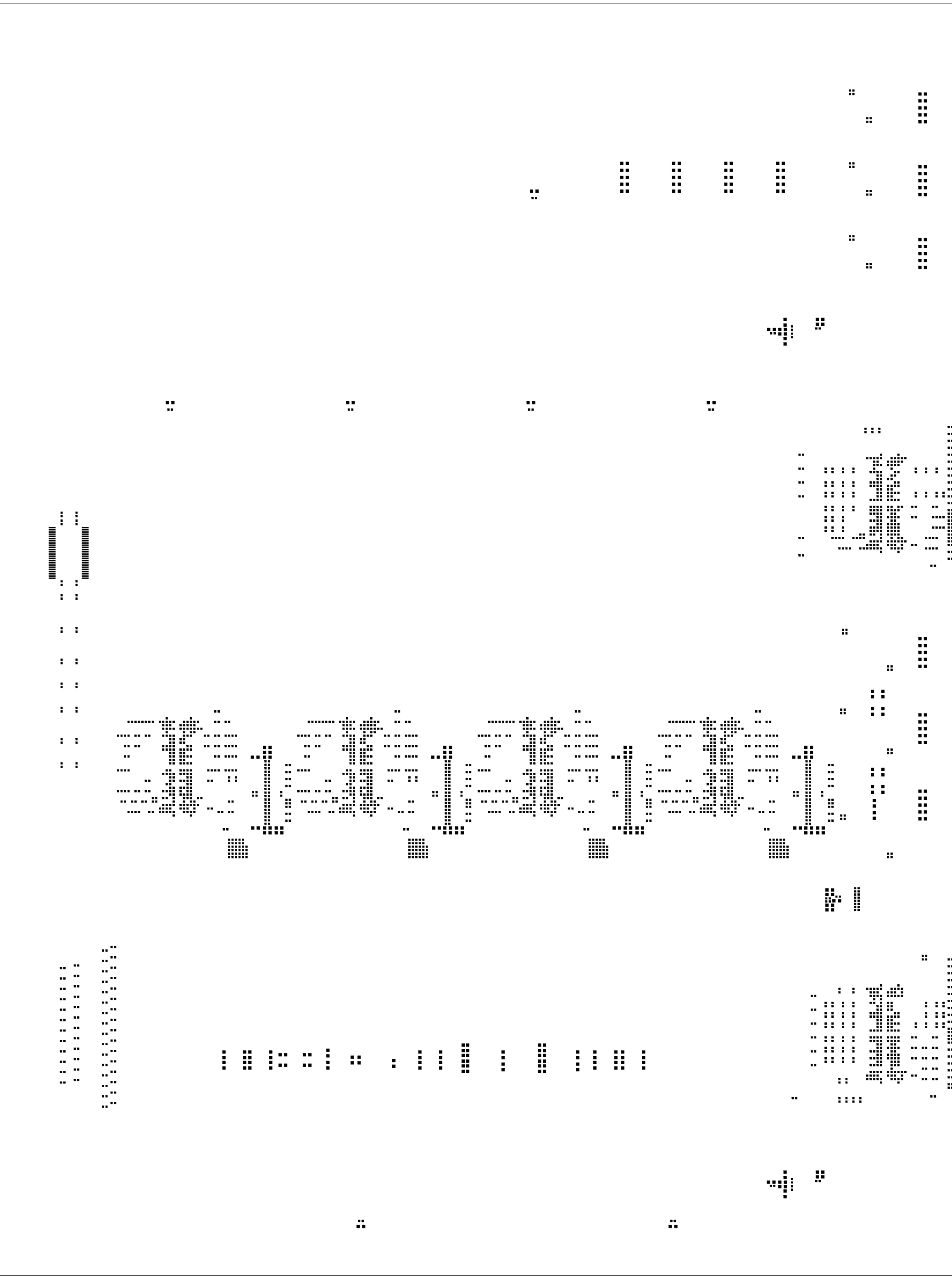

FTK Rear VME Test Card  
 March 25, 2013  
 8:49 am  
 Mircea Bogdan  
 Electronics Design Group  
 University Of Chicago

Sch. Draw 2808 Rev A  
 Spc. Draw 2809 Rev A  
 Asy. Draw 2810 Rev A

Artwork\_22: Bot Pastemask